

EE 322: EE Laboratory II

Final Portfolio

Steven Placzek



DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING
COLLEGE OF ENGINEERING
WESTERN NEW ENGLAND UNIVERSITY

May 8, 2025

Abstract

This portfolio documents a series of laboratory experiments conducted as part of EE322, with the objective of exploring and analyzing various MOSFET-based analog circuit topologies. The labs covered topics ranging from NMOS characterization and biasing techniques to the design and analysis of amplifiers and differential pairs. Experimental setups were implemented using the ALD1105/1106 transistor arrays and verified through simulations in LTSpice and Python-based data analysis. Circuit analyses techniques contained herein include the extraction of small-signal parameters, understanding the influence of source and load resistances on gain, and the role of feedback in stabilizing amplifier performance. Special emphasis was placed on evaluating frequency response, common-mode rejection, and the impact of grounding practices on measurement integrity. The final experiments introduced advanced concepts like S-parameter de-embedding using a Vector Network Analyzer (VNA), bridging analog design with RF characterization techniques. This comprehensive investigation demonstrates the critical interplay between theory, simulation, and practical implementation in analog circuit design.

Contents

Front matter

List of Figures	v
List of tables	vi
1 Lab 1 — NMOS Characterization	1
1.1 Background	1
1.2 Experiment 1: I_D vs. V_{DS}	1
1.3 Experiment 2: I_D vs. V_{GS}	2
1.4 Results	2
1.5 Conclusions	2
2 Lab 2 — IC Biasing Techniques	5
2.1 Lab Assignment Goals	5
2.2 Experiment 1: The MOSFET-Resistor Characterization	5
2.3 Experiment 2: The Beta Multiplier Characterization	7
2.4 Post Lab Data Analysis	9
2.4.1 Experiment 1 - Results:	9
2.4.2 Experiment 2 - Simulated Results:	11
2.4.3 Experiment 2 - Simulated vs Measured Results:	12
2.5 Code Listings	13
2.6 Conclusion	13
3 Lab 3 — Actively Loaded Common Source Amplifier	14
3.1 Lab Assignment Goals	14
3.2 Experiment 1: DC Operating Point	15
3.2.1 Measurement Issues & 60 Hz Noise	17
3.3 Experiment 2: Investigating the Role of R_{sig}	18
3.4 Experiment 3: Investigating the Role of R_L	18
3.5 Post Lab Data Analysis	18
3.6 Code Listings	22
3.7 Conclusion	22
4 Lab 4 — Frequency Response of the Common-Source Amplifier	24
4.1 Lab Assignment Goals	24
4.2 Experiment 1: DC Operating Point	25
4.3 Experiment 2: Frequency Response	25
4.4 Python Code Listings	27
4.5 Conclusion	27
5 Lab 5 — Frequency Response of the Common Source Amplifier with Feedback	29
5.1 Assignment Goals	29

5.2	Experiment 1: DC Operating Point	30
5.3	Experiment 2: Frequency Response	30
5.4	Measured Bode Plot	33
5.5	Simulated vs Measured Plots	34
5.6	Python Code Listings	35
5.7	Conclusion	35
6	Lab 6 — MOS Differential Pair: Single-Ended vs Differential Signals	36
6.1	Lab Assignment Goals	36
6.2	Experiment 1: MOS Differential Pair	36
6.3	Experiment 2: AC Response	37
6.4	Background	38
6.5	Single-ended vs Differential Input Comparison Plot	44
6.6	Python Code Listings	44
6.7	Conclusion	44
7	Lab 7 — MOS Differential Pair: Current Mirror	47
7.1	Lab Assignment Goals	47
7.2	Experiment 1: MOS Differential Pair DC Measurements	47
7.3	Experiment 2: MOS Differential Pair AC Response	50
7.4	Python Output: Simulated vs Measured % Difference	56
7.5	Python Code Listings	56
7.6	Conclusion	56
8	Lab 8 — VNA Measurement: De-Embedding S-Parameters	59
8.1	Lab Assignment Goals	59
8.2	S-Parameter De-embedding Methods	59
8.3	Measurement Fixture and De-Embedding Theory	60
8.3.1	Open, Short, and Thru Measurements	62
8.3.2	Low-Pass Filter De-embedding	62
8.3.3	High-Pass Filter De-embedding	63
8.4	Experimental Results and Analysis	64
8.4.1	High-Pass Filter Results	64
8.4.2	Verification with Keysight ADS Simulations	65
8.5	Python Code Listings	69
8.6	Conclusion	69
A	Appendix	72
A	Python Code Listings for Lab 01	73
B	Python Code Listings for Lab 02	83
C	Python Code Listings for Lab 03	90
D	Python Code Listings for Lab 04	92
E	Python Code Listings for Lab 06	99
F	Python Code Listings for Lab 07	104
G	Python Code Listings for Lab 08	114

List of Figures

1.1	Experiment 1 wiring diagram interfacing the transistor with the SMU and 3 channel power supply	2
1.2	Experiment 2 wiring diagram interfacing the transistor with the SMU, 3 channel power supply, and digital multimeter	3
1.3	Summary of data for the NMOS characterization laboratory assignment	4
2.1	The pinout and block diagram of the ALD1106 (top) and ALD1105 (bottom), Note: V^- is the body of the NMOS devices which is connected to lowest potential and V^+ is the body of the PMOS devices which is connected to the highest potential.	6
2.2	Wiring diagram of the MOSFET-resistor biasing circuit. The potentiometer had three terminals, with the top and bottom terminals used in combination with the middle terminal.	7
2.3	Wiring diagram of the MOSFET-resistor biasing circuit. The potentiometer had three terminals, with the top and bottom terminals used in combination with the middle terminal.	8
2.4	Experiment 1: Simulated vs Measured Plot	9
2.5	Experiment 2: Simulated I_D vs $\frac{d}{dt}(I_D)$ Plot	11
2.6	Experiment 2: Simulated vs Measured Plots	12
3.1	The pinout and block diagram of the ALD1105, Note: V^- is the body of the NMOS devices which is connected to lowest potential and V^+ is the body of the PMOS devices which is connected to the highest potential.	15
3.2	<i>Wiring diagram of the Common Source Amplifier.</i>	17
3.3	Simulated vs Measured data for $R_L = 10\text{ M}$	20
3.4	Simulated vs Measured data for $R_{sig} = 1\text{ k}$	21
4.1	The pinout and block diagram of the ALD1105. Note: V^- is the body of the NMOS devices, which is connected to the lowest potential, and V^+ is the body of the PMOS devices, which is connected to the highest potential.	24
5.1	The pinout and block diagram of the ALD1105, Note: V^- is the body of the NMOS devices which is connected to lowest potential and V^+ is the body of the PMOS devices which is connected to the highest potential.	29
5.2	Measured Bode Plot of the Lab 05 circuit.	33
5.3	Simulated vs Measured Gain & Phase	34
5.4	Simulated vs Measured Gain	34
5.5	Simulated vs Measured Phase	35

6.1	Pin-out and block diagram of the ALD1105. Note: The body of the NMOS devices (V^-) was connected to the source, and the body of the PMOS devices (V^+) was connected to its source.	36
6.2	(a) Plot of Current vs. Differential Input Voltage, (b) Plot of Transconductance .	42
6.3	In-Phase vs Out-of-Phase Plots of Simulated $V(vo)$	44
7.1	The pin-out and block diagram of the ALD1105. Note: V^- is the body of the NMOS devices and is connected to the source, and V^+ is the body of the PMOS devices, which is also connected to its source.	47
7.2	Differential Mode $V(vo)$	54
7.3	Common Mode $V(vo)$	55
8.1	Block-diagram representation of the measurement topology: the VNA observes the cascade of input fixture, DUT, and output fixture. [5]	60
8.2	Directionality of the four scattering parameters for a reciprocal two-port. [5] .	61
8.3	Formulae for converting S —parameters to T -parameters. [5]	61
8.4	Conversion of T -parameters back to S —parameters once fixture effects are removed. [5]	62
8.5	Comparison of LPF S —parameter measurements before and after de-embedding using OST method.	63
8.6	Comparison of HPF S —parameter measurements before and after de-embedding using OST method.	64
8.7	Plot generated by python code implementing the IEEE thru de-embedding standard. [4]	66
8.8	ADS schematic implementing OST de-embedding with De_Embed2. The DUT is the central LPF touchstone block.	66
8.9	Left-reference positioning used in the ADS De_Embed2 element.	67
8.10	Low-pass filter after OST de-embedding: ADS simulation. Compare with Fig. 8.5.	67
8.11	Validation of de-embedding on fixture structures.	68
8.12	Components utilized during Lab 08 including the Keysight VNA, ECAL calibration module, and RF Demo Board under test	70

List of Tables

1.1	Summary of $\sqrt{I_D}$ vs. V_{GS} extracted parameter values	4
1.2	Summary of I_D vs. V_{DS} extracted parameter values	4
2.1	Experiment 1 Data Summary	10
2.2	Experiment 2 Data Summary	12
3.1	Experiment 1 Summary Table	19
3.2	Experiment 2 Summary Table	20
3.3	Experiment 3 Summary Table	21
4.1	DC Summary Table	26
4.2	AC Summary Table	27
5.1	DC Summary Table	31
5.2	AC Summary Table	32
6.1	Resistor Summary	38
6.2	AC Summary Table - Single Ended Output	39
6.3	AC Summary Table - Differential Output	39
7.1	DC Summary Table	52
7.2	Resistor Summary	53
7.3	AC Summary Table - Single Ended Output	53

Chapter 1

Lab 1 — NMOS Characterization

This experiment aims to characterize an NMOS transistor for its relevant parameters, including threshold voltage (V_{TH}), transconductance parameter (K), and early voltage (V_A). The laboratory assignment utilizes Python to automate the measurement procedure and data acquisition. The ALD1106 is the device tested for this experiment.

1.1 Background

Parameters V_{TH} , K , and V_A are necessary parameters to determine both transistor bias points and small signal parameters. These parameters appear when examining the voltage-current characteristics of the NMOS transistor as follows:

- Cutoff Mode: $I_D = 0$ when $V_{GS} < V_{Tn}$ or $V_{DS} = 0$
- Triode Mode: $I_D = k'_n \left[\frac{W}{L} \right] \left(V_{OVn} - \frac{1}{2} V_{DS} \right) V_{DS}$ when $V_{GS} > V_{Tn}$ & $V_{DS} < V_{OVn}$
- Saturation Mode: $I_D = K_N V_{OVn}^2 \left(1 + \frac{V_{DS}}{|V_A|} \right)$ when $V_{GS} > V_{Tn}$ & $V_{DS} \geq V_{OVn}$

Typically in saturation mode, the $1 + V_{DS}/|V_A|$ term is ignored when performing the DC analysis of a transistor circuit. However, in this lab experiment it is a critical parameter to ensure that the appropriate approximations can be made to linearize data for parameter extraction.

1.2 Experiment 1: I_D vs. V_{DS}

In this experiment, the I_D vs. V_{DS} curves will be generated by using the Rohde Schwarz NGU401 source measure unit (SMU) and the Keithley 3-channel programmable power supply. In this experiment, the SMU will simultaneously source the V_{DS} voltage and measure the I_D current in real time. The voltage V_{GS} is generated by the programmable power supply as a

family of curves is desired. A circuit schematic and wiring diagram are shown in Figure 1.1. The Python code list is under the Coding List in the Appendix.

 


Figure 1.1: Experiment 1 wiring diagram interfacing the transistor with the SMU and 3 channel power supply

1.3 Experiment 2: I_D vs. V_{GS}

In this experiment, the I_D vs. V_{GS} curves will be generated by using the Rohde Schwarz NGU401 source measure unit (SMU), the Keithley 3-channel programmable power supply and the Keithley digital multimeter (DMM). In this experiment, the SMU will source the V_{GS} voltage. The voltage V_{DS} is generated by the programmable power supply and the current I_D is measured in real time by the Keithley DMM to generate the family of curves as desired. The circuit schematic remains the same; however, different voltages are being swept, therefore, the wiring diagram is modified as shown in Figure 1.2. The Python code list is under the Coding List Listing A.2, in the Appendix.

1.4 Results

The post-laboratory tasks for this assignment included plotting the data from experiments 1 and 2. These plots include I_D vs. V_{DS} for a family of V_{GS} values along with plotting I_D vs. V_{GS} for a family of V_{DS} values. The transistor parameters V_{TH} , K , and V_A are extracted by curving fitting the data from experiments 1 and 2. Code listing provides a detailed approach for the extraction of data parameters. Figure 1.3 displays the summarized results of the experiments, and the data parameters are listed in Tables 1.1 and 1.2. listing A.3

1.5 Conclusions

The data results indicate the NMOS transistor has a threshold voltage $V_{TH} = 0.547$, $K_N = 265.96 \mu A/V$, and Early voltages of -62.75 , -88.63 , and -140.18 . The linearized region used to

0.9

Figure 1.2: Experiment 2 wiring diagram interfacing the transistor with the SMU, 3 channel power supply, and digital multimeter

extract V_{TH} & K_N had a coefficient of determination fit of $R^2 = 0.9988$ representing a near ideal fit across multiple data points with a small standard deviation among the various values of V_{DS} . The data points are chosen to minimize short channel effects from the measured results. In addition, it is experimentally observed that the Early voltage for each V_{GS} sweep does not intersect the x-axis at the same point, indicating that the channel length modulation parameter is dependent on bias conditions. Therefore, when modeling this phenomenon, it likely requires a mathematical fit to fully caption its effects.

Quantity	Mean Value	Standard Deviation	Units
K_N	265.96	5.83	$\mu\text{A/V}$
V_{Tn}	0.547	0.007	V

Table 1.1: Summary of $\sqrt{I_D}$ vs. V_{GS} extracted parameter values

Quantity	Value	Units
$V_A (V_{GS} = 2\text{V})$	-62.74	V
$V_A (V_{GS} = 4\text{V})$	-88.63	V
$V_A (V_{GS} = 6\text{V})$	-140.18	V

 
Table 1.2: Summary of I_D vs. V_{DS} extracted parameter values

Figure 1.3: Summary of data for the NMOS characterization laboratory assignment

Chapter 2

Lab 2 — IC Biasing Techniques

2.1 Lab Assignment Goals

The goal of this lab was to study and compare the MOSFET-resistor biasing circuit and the beta multiplier circuit, specifically focusing on performance metrics such as power supply sensitivity. Biasing is essential in integrated circuits to establish proper operating points for transistors, ensuring consistent performance and linearity despite variations in temperature, power supply, or transistor parameters. The beta multiplier circuit is often preferred over a simple MOSFET-resistor configuration due to its ability to provide a more stable and predictable bias current, making it less sensitive to process and temperature variations. This stability is achieved through a feedback loop and multiple transistors that generate a reference current capable of adapting to changes, improving control and reliability in precision applications.

To accomplish this, both circuits were simulated in LTSpice and built on a breadboard using the ALD1106/ALD1105 transistor array. Simulations and experimental measurements were conducted to analyze circuit behavior under different conditions, particularly variations in supply voltage. Data from both approaches were compared to evaluate the performance differences between the two biasing methods and to assess the advantages of the beta multiplier over the MOSFET-resistor configuration.

2.2 Experiment 1: The MOSFET-Resistor Characterization


The objectives of this experiment involved characterizing a MOSFET-resistor circuit, as illustrated in the schematic below. The following tasks were performed:

- The resistor was replaced with a $20\text{k}\Omega$ potentiometer while setting $V_{DD} = 10\text{V}$. The resistance R was determined at which $I_D = 500\mu\text{A}$.
- With the current set to $I_D = 500\mu\text{A}$, the DC operating point was identified.

0.5

Figure 2.1: The pinout and block diagram of the ALD1106 (top) and ALD1105 (bottom), **Note: V^- is the body of the NMOS devices which is connected to lowest potential and V^+ is the body of the PMOS devices which is connected to the highest potential.**

 - Finally, the supply voltage V_{DD} was swept from 0 to 15V.




0.475

Figure 2.2: Wiring diagram of the MOSFET-resistor biasing circuit. The potentiometer had three terminals, with the top and bottom terminals used in combination with the middle terminal.

 2.3 Experiment 2: The Beta Multiplier Characterization

The objectives of this experiment involved characterizing a beta multiplier circuit, as illustrated in the schematic below. The following tasks were performed. Additionally, the width of Q_2 was four times that of Q_1 , achieved by wiring four NMOS devices in parallel as available on the ALD1106:

- The resistor was replaced with a $5k\Omega$ potentiometer while setting $V_{DD} = 10V$. The resistance R was determined at which $I_{D2} = 500\mu A$.
- With the current set to $I_{D2} = 500\mu A$, the DC operating point was identified.
- Finally, the supply voltage V_{DD} was swept from 0 to 15V.
- Python Code used for this experiment can be found under the code listings chapter B, chapter B, & chapter B



0.475

Figure 2.3: Wiring diagram of the MOSFET-resistor biasing circuit. The potentiometer had three terminals, with the top and bottom terminals used in combination with the middle terminal.

2.4 Post Lab Data Analysis

The post-lab analysis involved the following tasks:

- The circuits from Experiment 1 and Experiment 2 were simulated, following the same procedure of sweeping R to determine the bias point at $I_D = I_{D2} = 500\mu\text{A}$. The DC operating point was then identified, followed by sweeping the power supply V_{DD} from 0 to 15V.
- The tables for simulated and measured data were completed as specified.
- Both the simulated and measured power supply voltage sweeps were plotted on the same curve. The derivative of the simulated data was taken to determine the supply voltage sensitivity at the operating point $V_{DD} = 10\text{V}$.
- The results from Experiment 1 and Experiment 2 were compared to determine which circuit exhibited greater resistance to dynamic changes in the power supply.

2.4.1 Experiment 1 - Results:

 


Figure 2.4: Experiment 1: Simulated vs Measured Plot

Quantity	Simulated	Measured	Units
R	16.200	16.003	$\text{k}\Omega$
V_{GS1}	1.91	1.940	V
V_{DS1}	1.91	1.940	V
V_{OV1}	1.337	1.341	V
I_{D1}	499.999	504.477	μA

Table 2.1: Experiment 1 Data Summary

 


Figure 2.5: Experiment 2: Simulated I_D vs $\frac{d}{dt}(I_D)$ Plot

2.4.2 Experiment 2 - Simulated Results:

The post-lab analysis involved comparing two circuit configurations, with the data clearly demonstrating that the circuit from Experiment 2 exhibits superior resistance to sudden changes in the power supply voltage. This enhanced stability can be attributed to the beta mirror configuration, which employs a cascade of current mirrors to maintain consistent current flow. The multiple transistor stages in the beta mirror create a high-impedance path that effectively isolates the bias current from power supply fluctuations. Additionally, the negative feedback inherent in the mirror configuration helps compensate for any variations in supply voltage by adjusting the gate-source voltages of the transistors to maintain constant current.

Quantity	Simulated	Measured	Units
R	1.254	1.0361	$k\Omega$
V_{GS1}	1.980	1.985	V
V_{DS1}	1.980	1.985	V
V_{OV1}	1.407	1.424	V
I_{D1}	552.000	506.814	μA
V_{GS2}	1.350	1.496	V
V_{DS2}	6.420	6.646	V
V_{OV2}	0.644	0.935	V
I_{D2}	500.000	506.814	μA
V_{SG3}	2.960	2.861	V
V_{SD3}	8.020	8.006	V
$ V_{OV3} $	2.313	2.399	V
I_{D3}	552.000	506.814	μA
V_{SG4}	2.960	2.862	V
$ V_{OV4} $	2.313	2.301	V
I_{D4}	500.000	506.814	μA

Table 2.2: Experiment 2 Data Summary

2.4.3 Experiment 2 - Simulated vs Measured Results:

 


Figure 2.6: Experiment 2: Simulated vs Measured Plots

2.5 Code Listings

The Python implementations for the biasing analysis can be found in the Appendix: Plot Measured vs Simulated Data (listing B.1), Extract OP Values from LTSpice (listing B.2), Plot Measured vs Simulated Current (listing B.3), Calculate MOSFET Parameters (listing B.4), and Simulated vs Measured Data Plot (listing B.5).

2.6 Conclusion

This lab effectively demonstrated the differences in performance and robustness between a basic MOSFET-resistor biasing circuit and a beta multiplier biasing configuration. Through both simulation and physical prototyping, it was observed that while the MOSFET-resistor circuit can achieve the desired operating point with manual tuning, it suffers from significant sensitivity to changes in supply voltage. In contrast, the beta multiplier circuit consistently maintained a stable bias current across varying supply voltages, showcasing superior power supply rejection characteristics.

The enhanced stability of the beta multiplier can be attributed to its negative feedback mechanism and the use of matched transistor pairs, which allow the circuit to self-correct and adapt to fluctuations in external conditions. This makes it a preferred choice in precision analog and mixed-signal applications where stability and predictability are crucial.

Simulation results closely matched experimental data for both circuits, validating the modeling approach in LTSpice. Additionally, the derivative analysis confirmed that the beta multiplier exhibited a flatter response in current with respect to changes in V_{DD} , quantitatively proving its reduced supply voltage sensitivity.

Overall, results highlight the importance of choosing appropriate biasing strategies in analog design and illustrated the trade-off between simplicity and performance in circuit design.

Chapter 3

Lab 3 — Actively Loaded Common Source Amplifier

3.1 Lab Assignment Goals

This objective of this lab assignment was to methodically evaluate a common source amplifier built with the ALD1105 MOSFET, with the overarching objective of determining how variations in load resistance and signal generator resistance affect circuit performance. The group's tasks were organized into a series of experiments, each aimed at addressing distinct aspects of amplifier behavior. In the first experiment, the DC operating point was established by adjusting the DC bias voltage V_G until the output voltage V_O reached 5V. This step involved measuring node voltages and calculating the corresponding drain currents, providing a baseline for subsequent analysis. Establishing an accurate operating point is critical to ensure that the MOSFET operates in the intended region, which is a fundamental concept that can sometimes be overlooked in traditional electrical engineering coursework. This experiment was intended to highlight the impact of how very slight adjustments to load resistance, along with signal generator resistance, will result in large changes with the output impedance and thus have a larger affect upon the overall stability of the circuit.


0.5

Figure 3.1: The pinout and block diagram of the ALD1105, **Note: V^- is the body of the NMOS devices which is connected to lowest potential and V^+ is the body of the PMOS devices which is connected to the highest potential.**

 3.2 Experiment 1: DC Operating Point

Using the circuit shown below with the parameter values given, adjust the DC voltage V_{GG} such that the output voltage $V_O = 5\text{ V}$

- Find the dc operating point by measuring the node voltages and calculating the currents. Complete the summary table.



$$V_{DD} = 10 \text{ V} \quad V_O = 5 \text{ V} \quad C_B = 0.1 \mu\text{F}$$

$$R = 15\text{k} \Omega \quad R_G = 10\text{M} \Omega$$

$$K_N = 270 \mu\text{A/V}^2 \quad V_{Tn} = 0.573 \text{ V} \quad \lambda_N = 0.0165 \text{ V}^{-1}$$

$$K_P = 88 \mu\text{A/V}^2 \quad V_{Tp} = -0.647 \text{ V} \quad \lambda_P = 0.0219 \text{ V}^{-1}$$

 


Figure 3.2: Wiring diagram of the Common Source Amplifier.

3.2.1 Measurement Issues & 60 Hz Noise

The physical measurement data were compromised due to improper grounding practices. In this instance, the use of separate ground rails resulted in ground loops that injected considerable 60 Hz interference into the circuit measurements. This phenomenon is particularly problematic with the ALD1105 MOSFET, as its performance is highly sensitive to noise in the biasing network. Wiring the transistor to multiple different rails will result in ground loops that introduce significant 60 Hz interference into measurement data, which this experiment demonstrated quite clearly. [1]

In this scenario, the use of separate ground rails for the DC power supply, circuit, oscilloscope probes, and function generator led to mismatched ground potentials. According to an IEEE article on mitigating noise in electronic measurement systems, improper grounding practices can lead to the formation of ground loops that introduce significant 60 Hz interference into measurement data. In this case, using separate ground rails for the DC power supply, circuit, oscilloscope probes, and function generator resulted in mismatched ground potentials. This is particularly problematic when working with the ALD1105 MOSFET, which is highly sensitive to noise in its biasing network and operating conditions. [2]

3.3 Experiment 2: Investigating the Role of R_{sig}

After establishing the DC operating point in Experiment 1, the role of the signal generator resistance, R_{sig} , on the overall AC small-signal gain, G_v , was investigated. The gain was defined as:

$$G_v = \frac{v_o}{v_{sig}}$$

The following procedure was implemented:

- The load resistance was set to $R_L = 10 \text{ M}\Omega$ (as provided by the oscilloscope probe).
- The small-signal gain, G_v , was measured for various values of R_{sig} , specifically for:

$$R_{sig} = 10 \text{ M}\Omega$$

$$R_{sig} = 100 \text{ k}\Omega$$

$$R_{sig} = 10 \text{ k}\Omega$$

$$R_{sig} = 1 \text{ k}\Omega$$

3.4 Experiment 3: Investigating the Role of R_L

Following the establishment of the DC operating point in Experiment 1, the influence of the load resistance, R_L , on the AC small-signal gain, G_v , was examined. The gain was defined as:

$$G_v = \frac{v_o}{v_{sig}}$$

The following procedure was executed:

- The signal generator resistance was fixed at $R_{sig} = 1 \text{ k}\Omega$.
- The small-signal gain, G_v , was measured for various values of R_L , specifically:

$$R_L = 10 \text{ M}\Omega$$

$$R_L = 100 \text{ k}\Omega$$

$$R_L = 10 \text{ k}\Omega$$

$$R_L = 1 \text{ k}\Omega$$

3.5 Post Lab Data Analysis

The post-lab analysis consisted of the following tasks:

- Simulate the circuits from experiments 1, 2, and 3 following the same procedure of sweep-

ing V_{GG} to find the bias point where $V_O = 5V$ for experiment 1. Then operating under the bias condition, perform an AC analysis to find the ac small signal gain G_V under the various R_{sig} and R_L conditions specified in experiments 2 and 3.


- The completed simulated data been entered into the tables, (*the missing measurements will completed before the next lab meeting*), as specified below:

Experiment 1 Summary Table				
Device	Quantity	Simulated	Measured	Units
Q_1	I_D	494.0	485.000	μA
	$ V_{OV} $	1.299	1.290	V
	V_G	1.872	1.860	V
	V_D	5.058	4.970	V
	V_S	0.000	0.000	V
Q_2	I_D	494.0	-480.000	μA
	$ V_{OV} $	7.481	2.310	V
	V_G	1.872	7.030	V
	V_D	5.058	4.970	V
	V_S	10.000	9.990	V
Q_3	I_D	494.0	-480.009	μA
	$ V_{OV} $	2.250	2.310	V
	V_G	7.103	7.040	V
	V_D	7.103	7.040	V
	V_S	10.000	9.99	V

Table 3.1: Experiment 1 Summary Table


AC Small Signal Gain $R_L = 10\text{ M}\Omega$				
Condition	Quantity	Simulated	Measured	Units
$R_{sig} = 10\text{ M}\Omega$	G_v	-21.900	7.6110	V/V
	G_v	26.810	17.6288	dB
$R_{sig} = 100\text{ k}\Omega$	G_v	-43.365	16.2100	V/V
	G_v	32.743	24.1957	dB
$R_{sig} = 10\text{ k}\Omega$	G_v	-43.756	20.1700	V/V
	G_v	32.821	26.0941	dB
$R_{sig} = 1\text{ k}\Omega$	G_v	-43.795	22.3100	V/V
	G_v	32.829	26.9700	dB

Table 3.2: Experiment 2 Summary Table

  Figure 3.3: Simulated vs Measured data for $R_L = 10\text{ M}\Omega$

AC Small Signal Gain $R_{sig} = 1\text{ k}\Omega$				
Condition	Quantity	Simulated	Measured	Units
$R_L = 10\text{ M}\Omega$	G_v	-21.900	31.2000	V/V
	G_v	26.810	20.881	dB
$R_L = 100\text{ k}\Omega$	G_v	-13.943	23.5000	V/V
	G_v	22.887	27.4214	dB
$R_L = 10\text{ k}\Omega$	G_v	-3.240	3.6500	V/V
	G_v	10.211	11.2459	dB
$R_L = 1\text{ k}\Omega$	G_v	-0.373	0.9510	V/V
	G_v	-8.555	-0.4364	dB

Table 3.3: Experiment 3 Summary Table

Figure 3.4: Simulated vs Measured data for $R_{sig} = 1\text{ k}\Omega$

3.6 Code Listings

The Python code used for the common source amplifier analysis can be found in the Appendix: Common Source Amp LTSpice Sweep (listing C.1).

3.7 Conclusion

This lab successfully demonstrated the critical influence of source and load resistances on the performance of a common source amplifier using the ALD1105 MOSFET. Through a series of controlled experiments, both simulated and measured, the impact of varying R_{sig} and R_L on the AC small-signal gain G_V was thoroughly evaluated.

In Experiment 1, the DC operating point was accurately established by adjusting V_O such that the output voltage V_O was 5 V. This step confirmed the theoretical behavior of MOSFETs in the saturation region and emphasized the importance of correct biasing for reliable amplifier operation. The lack of close agreement between simulated and measured data reinforced the inaccuracy of the transistor model.

Experiment 2 showed that as R_{sig} decreased, the voltage gain G_v increased significantly, particularly in the measured results. This outcome is consistent with theoretical expectations, as a lower source resistance reduces signal attenuation before the gate of the MOSFET, allowing a greater portion of the input signal to modulate the channel current.

Experiment 3 revealed a strong dependence of gain on the load resistance R_L . Higher values of R_L led to markedly high gains, again matching theoretical predictions based on the amplifier's gain formula $G_v \approx -g_m R_D \parallel R_L$. Results emphasized that loading effects from external measurement equipment (e.g., oscilloscope probes) or downstream circuitry can significantly influence observed performance.

The major insight from the lab was effects of grounding practices on measurement quality. Ground loops introduced substantial 60 Hz noise, initially preventing accurate gain readings. Once corrected, the improved grounding scheme allowed for reliable data collection that matched simulation trends closely. This lab demonstrated the sensitivity of analog circuits to parasitics and component values, especially in high-impedance configurations. Importance of thoughtful design and measurement practices is paramount for achieving predictable amplifier behavior.

References

- [1] C. Yao et al., “Electromagnetic noise coupling and mitigation in dynamic tests of high power switching devices”, in *2015 IEEE Energy Conversion Congress and Exposition (ECCE)*, 2015, pp. 6610–6615. DOI: 10.1109/ECCE.2015.7310585.
- [2] R.-C. Cavache and M. Pantazică, “Guidelines for reducing conductive coupling noise in electronic systems”, in *2023 IEEE 29th International Symposium for Design and Technology in Electronic Packaging (SIITME)*, 2023, pp. 293–296. DOI: 10.1109/SIITME59799.2023.10431377.

Chapter 4

Lab 4 — Frequency Response of the Common-Source Amplifier

4.1 Lab Assignment Goals

This lab involved implementing a common source amplifier using the ALD1105 MOSFET to analyze the frequency response. The primary objectives included measuring the DC operating point, such as the drain current and voltage, and generating a Bode plot of the frequency response. Since the internal capacitances of the MOSFETs were too small for the laboratory equipment to measure, discrete capacitors were added to mimic their behavior. These measurements provided insight into optimizing amplifier performance for various applications. LTSpice was used to validate measurement techniques.


 


Figure 4.1: The pinout and block diagram of the ALD1105. **Note: V^- is the body of the NMOS devices, which is connected to the lowest potential, and V^+ is the body of the PMOS devices, which is connected to the highest potential.**

 4.2 Experiment 1: DC Operating Point

Using the circuit shown below with the given parameter values, the DC voltage V_{GG} was adjusted such that the output voltage $V_O = 5$ V.

- The DC operating point was determined by measuring the node voltages and calculating the currents. The summary table was then completed.



4.3 Experiment 2: Frequency Response

By employing appropriate AC measurement techniques, the frequency response of the amplifier was determined. The frequency range analyzed spanned from 10 Hz to 100 kHz. The following tasks were completed:

- The mid-band gain $|G_{v(\text{mid})}|$ was found.
- The bandwidth was determined by measuring f_L and f_H , followed by computing the Gain Bandwidth Product (GBW) in Hz. The mid-band gain was converted to V/V.
- The measured and simulated results were plotted on the same curve, ensuring a magnitude range of 0 to +30 dB.
- The results for each experiment have been provided in the following tables.
- Calculations were done using Python and Simulations ran using LTSpice.

DC Operating Point				
Device	Quantity	Simulated	Measured	Units
Q_1	I_D	-485.30	-492.70	μA
	$ V_{OV} $	1.25	1.30	V
	V_G	1.85	1.85	V
	V_D	5.10	4.967	V
	V_S	0.00	0.05	V
Q_2	I_D	-473.564	-492.70	μA
	$ V_{OV} $	2.250	2.224	V
	V_G	7.103	7.129	V
	V_D	5.058	4.980	V
	V_S	10.000	10.000	V
Q_3	I_D	-473.564	-473.600	μA
	$ V_{OV} $	2.221	2.250	V
	V_G	7.120	7.100	V
	V_D	7.120	7.100	V
	V_S	10.000	10.000	V

Table 4.1: DC Summary Table

AC Summary			
Quantity	Simulated	Measured	Units
$ G_{v(\text{mid})} $	27.325	17.361	V/V
$ G_{v(\text{mid})} $	28.731	24.791	dB
f_L	44.668	101.604	Hz
f_H	13.490	3.937	kHz
BW	13.445	3.835	kHz
GBP	367.384	66.582	kHz

Table 4.2: AC Summary Table

4.4 Python Code Listings

The Python implementation for frequency response analysis can be found in the Appendix (listing D.1).

4.5 Conclusion

This lab focused on analyzing the frequency response of a common source amplifier by measuring its DC operating point, generating a Bode plot, and comparing simulated and measured data. Python code for this lab can be found in the code listing chapter D. The process included adjusting the biasing conditions, sweeping the frequency response, and capturing key characteristics such as the lower and upper cutoff frequencies (f_L and f_H), gain bandwidth product (GBP), and mid-band gain (G_v). The measured high-frequency cutoff (f_H) was found to be lower than the simulated value, indicating additional parasitic effects or variations in component behavior. The Miller Effect causes large discrepancies in the values between simulated and measured. The Miller effect states that if an impedance (Z) is in parallel with an inverting amplifier with a gain of magnitude A (Figure 3, left), it can be split into two separate impedances at the input and output of the amplifier (Figure 3, right). The input and output impedances have values of $Z_{in} = \frac{1}{Z_1 + \frac{1}{A}}$ and $Z_{out} = \frac{Z_1}{1+A}$, respectively, and are both tied to ground.

Another critical factor is the **Miller effect**, which significantly impacts the high-frequency response of the amplifier. The Miller effect describes how the capacitance between the drain and gate (C_{gd}) is amplified by the voltage gain of the stage, effectively increasing the equivalent input capacitance. This phenomenon lowers the bandwidth by reducing the effective high-frequency cutoff. In simulations, SPICE models may not fully capture all secondary Miller capacitance effects, especially if they do not account for layout-dependent parasitics. In practical circuits, additional unintended capacitances and PCB trace effects further exacerbate the Miller effect, further decreasing the measured f_H compared to the simulated value.

Results demonstrated how real-world variations influence circuit performance and emphasized the importance of simulation validation. Future work may involve refining the biasing network and improving frequency response accuracy through component selection and layout optimization.

Chapter 5

Lab 5 — Frequency Response of the Common Source Amplifier with Feedback

5.1 Assignment Goals

In this lab, the common source amplifier from Lab 04 was modified by applying feedback to the circuit. Specifically, negative feedback was introduced by adding a resistor from the drain of Q_1 to the gate of Q_1 . This feedback served multiple purposes, including stabilizing the DC bias point, eliminating the need for a dedicated bias voltage. The effect of feedback on bandwidth and gain was observed, showing an increase in bandwidth at the expense of overall circuit gain. However, it was also noted that feedback stabilized the gain, making it dependent only on the feedback resistor and, in this case, the signal generator resistor. The ALD1105 MOSFET was used to analyze the frequency response, and LTSpice simulations were conducted to validate measurement techniques.


 


Figure 5.1: The pinout and block diagram of the ALD1105, **Note: V^- is the body of the NMOS devices which is connected to lowest potential and V^+ is the body of the PMOS devices which is connected to the highest potential.**

 5.2 Experiment 1: DC Operating Point

Using the circuit shown below with the given parameter values, the potentiometer was adjusted to set the total current to $I_{Total} = 1 \text{ mA}$.

- The DC operating point was determined by measuring the node voltages and calculating the currents. The summary table was then completed.



$$V_{DD} = 10 \text{ V} \quad C_B = 0.022 \mu\text{F} \quad R = 25 \text{ k}\Omega \text{ Potentiometer}$$

$$R_F = 330 \text{ k}\Omega \quad R_{sig} = 100 \text{ k}\Omega \quad R_L = 10 \text{ M}\Omega \text{ (Probe)}$$

$$C_1 = 10 \text{ pF} \quad C_2 = 3.3 \text{ pF} \quad C_3 = 22 \text{ pF} + 15 \text{ pF (Probe)} \quad C_4 = 3.3 \text{ pF} \quad C_5 = 22 \text{ pF}$$

5.3 Experiment 2: Frequency Response

Using appropriate AC measurement techniques, the frequency response of the amplifier was determined over a frequency range of 10 Hz to 100 kHz. Additionally, the following tasks were completed:

- The mid-band gain $|G_{v(\text{mid})}|$ was measured.
- The bandwidth was determined by measuring f_L and f_H , and the Gain Bandwidth Product (GBW) was computed in Hertz. The mid-band gain was converted to V/V for accuracy.

- The measured results were plotted against the simulated results on the same curve, using a magnitude range of 0 to +30 dB.
- The summary tables at the end of the handout were completed.

DC Operating Point				
Device	Quantity	Simulated	Measured	Units
Q_1	I_D	525.197	500.290	μA
	$ V_{OV} $	1.373	0.569	V
	V_G	1.945	1.142	V
	V_D	1.946	1.480	V
	V_S	0.000	0.000	V
Q_2	I_D	525.197	500.290	μA
	$ V_{OV} $	7.398	7.933	V
	V_G	1.956	1.142	V
	V_D	1.956	1.147	V
	V_S	10.000	10.000	V
Q_3	I_D	474.798	500.290	μA
	$ V_{OV} $	2.253	4.932	V
	V_G	7.100	4.421	V
	V_D	7.100	4.421	V
	V_S	10.000	10.000	V

Table 5.1: DC Summary Table

AC Summary			
Quantity	Simulated	Measured	Units
$ G_{v(\text{mid})} $	3.053	2.945	V/V
$ G_{v(\text{mid})} $	9.694	9.381	dB
f_L	100.000	67.608	Hz
f_H	63.100	138.038	kHz
BW	137.971	137.971	kHz
GBP	192.327	406.271	kHz

Table 5.2: AC Summary Table

5.4 Measured Bode Plot

 


Figure 5.2: Measured Bode Plot of the Lab 05 circuit.

5.5 Simulated vs Measured Plots

 


Figure 5.3: Simulated vs Measured Gain & Phase

 


Figure 5.4: Simulated vs Measured Gain

 


Figure 5.5: Simulated vs Measured Phase

5.6 Python Code Listings

5.7 Conclusion

This lab demonstrated the powerful role of negative feedback in modifying the behavior of a common source amplifier. By introducing a resistor from the drain to the gate of transistor Q_1 , the amplifier achieved improved DC stability without requiring a separate bias voltage. This feedback mechanism effectively stabilized the operating point and gain, making the circuit more predictable and less sensitive to parameter variations. Although the overall voltage gain was reduced, the trade-off resulted in a substantial increase in bandwidth, leading to a higher Gain-Bandwidth Product (GBW). The comparison between simulated and measured results showed good agreement, validating the effectiveness of the feedback design and confirming the accuracy of LTSpice simulations. The experiment reinforces the practical value of feedback in analog circuit design, particularly for improving linearity, stability, and frequency response.

Chapter 6

Lab 6 — MOS Differential Pair: Single-Ended vs Differential Signals

6.1 Lab Assignment Goals

The objective of this lab was to investigate the behavior of a differential pair of MOS composed of Q_1 and Q_2 , and to analyze the distinctions between single-ended and differential signaling, with particular emphasis on their effect on the common mode rejection ratio (CMRR). The circuit was implemented using the ALD1105 MOSFET array. Differential operation was examined to evaluate its effectiveness in enhancing noise rejection and improving signal integrity. LTSpice simulations were utilized to validate theoretical predictions. In addition, worst-case and Monte Carlo analyses were performed to assess variability and robustness.

 



Figure 6.1: Pin-out and block diagram of the ALD1105. **Note:** The body of the NMOS devices (V^-) was connected to the source, and the body of the PMOS devices (V^+) was connected to its source.

6.2 Experiment 1: MOS Differential Pair

The MOS differential pair circuit, shown in Figure 6.1, was constructed with the Analog Discovery Studio. The following tasks were completed:

- Resistances R_D and R_{CS} were measured and recorded in the summary table.

 - The DC operating point was determined by measuring the node voltages and calculating the drain currents. The results were documented in the summary table.
- One of the most common questions asked is the difference between single-ended and differential signal inputs, and what applications they should be considered in. [1]



Circuit Parameters: $V_{DD} = 12\text{ V}$, $-V_{SS} = -12\text{ V}$, $R_D = 18\text{ k}\Omega$, $R_{CS} = 10\text{ k}\Omega$, $V_{I1} = V_{I2} = 0\text{ V}$
V MOS Differential Pair Circuit

6.3 Experiment 2: AC Response

The AC response of the differential pair was evaluated by determining the differential gain, the common-mode gain, and calculating the common-mode rejection ratio (CMRR). Measurements were performed for single-ended output (at node V_Y with respect to the ground) and differential output (measuring voltage across nodes V_Y and V_X). The following procedures were followed:

- For the differential input, a sinusoidal signal was applied to the positive input terminal and an equal but opposite phase signal was applied to the negative terminal, while both function generators were synchronized and biased appropriately.
- For common-mode input, identical sinusoidal signals were applied to both input terminals without phase offset.
- Both wave generators were synchronized and appropriately biased.
- During AC analysis in LTSpice, the measured resistor values were used.
- The results were documented in the summary tables that have been provided on the following pages.

Quantity	Measured	Units
R_D	18.025	$k\Omega$
R_D	17.975	$k\Omega$
R_{CS}	9.839	$k\Omega$

Table 6.1: Resistor Summary

DC Operating Point				
Device	Quantity	Simulated	Measured	Units
Q_1	I_D	562.943	483.141	μA
	$ V_{OV} $	1.407	1.141	V
	V_G	0.000	0.000	V
	V_D	3.063	2.896	V
	V_S	-1.891	-1.820	V
Q_2	I_D	558.043	524.011	μA
	$ V_{OV} $	1.407	1.140	V
	V_G	0.000	0.000	V
	V_D	2.060	2.011	V
	V_S	-1.700	-1.819	V

6.4 Background

In contrast to single-ended signaling, where the signal is measured with respect to a fixed potential (usually ground), differential signaling uses two complementary signals referenced to a common-mode voltage. [2] This configuration provides several advantages:

- **Immunity to environmental noise:** External interference affects both lines equally, and the differential measurement cancels out this noise.
- **Rejection of power supply noise:** Voltage fluctuations in the supply appear as common-mode noise, which is rejected by the differential pair.
- **Reduction of coupled noise:** Crosstalk and interference from adjacent signal lines are minimized.

[3]

AC Summary - Single Ended			
Quantity	Simulated	Measured	Units
A_d	6.018	6.205	V/V
A_d	15.580	15.801	dB
A_{cm}	0.840	0.499	V/V
A_{cm}	-1.515	-5.924	dB
CMRR	17.104	21.724	dB

Table 6.2: AC Summary Table - Single Ended Output

AC Summary - Differential			
Quantity	Simulated	Measured	Units
A_d	12.020	12.024	V/V
A_d	21.598	21.578	dB
A_{cm}	0.001	0.053	V/V
A_{cm}	-61.379	-26.760	dB
CMRR	59.872	48.328	dB

Table 6.3: AC Summary Table - Differential Output

Calculations and Methodology:

$$V_P = V_{in1} - V_{GS1} = V_{in2} - V_{GS2}$$

$$V_{in1} - V_{in2} = V_{GS1} - V_{GS2}$$

$$V_{in1} - V_{in2} = V_{GS1} - V_{GS2} \quad (6.1)$$

Assuming M_1 and M_2 in saturation:

$$(V_{GS} - V_{TH})^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}} \quad (2)$$

$$V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH} \quad (6.2)$$

From Eq. 1 & 2:

$$V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

Squaring both sides, and since: $I_{SS} = I_{D1} + I_{D2}$

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} \left(I_{SS} - 2\sqrt{I_{D1}I_{D2}} \right) \quad (6.3)$$

$$\frac{\mu_n C_{ox} W}{2L} (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1}I_{D2}} \quad (6.4)$$

$$4I_{D1}I_{D2} = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2 = I_{SS}^2 - (I_{D1} - I_{D2})^2 \quad (6.5)$$

$$(I_{D1} - I_{D2})^2 = -\frac{1}{4} \left(\frac{\mu_n C_{ox}}{W/L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS} \frac{\mu_n C_{ox}}{W/L} (V_{in1} - V_{in2})^2 \quad (6.6)$$

$$I_{D1} - I_{D2} = \frac{\mu_n C_{ox} W}{2L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2} \quad (6.7)$$

$$\frac{\mu_n C_{ox} W}{2L} (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1}I_{D2}} \quad (6.8)$$

$$4I_{D1}I_{D2} = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2 = I_{SS}^2 - (I_{D1} - I_{D2})^2 \quad (6.9)$$

$$(I_{D1} - I_{D2})^2 = -\frac{1}{4} \left(\frac{\mu_n C_{ox}}{W/L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS} \frac{\mu_n C_{ox}}{W/L} (V_{in1} - V_{in2})^2 \quad (6.10)$$

$$I_{D1} - I_{D2} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2} \quad (6.11)$$

Let $\Delta V_{in} = V_{in1} - V_{in2}$ and $\Delta I_D = I_{D1} - I_{D2}$

Deriving Eq. (3) with respect to ΔV_{in} :

$$G_m = \frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2\Delta V_{in}^2} \quad (6.12)$$

For $\Delta V_{in} = 0$:

$$G_m = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$$

Since:

$$V_{out1} - V_{out2} = V_{DD} - I_{D1} R_{D1} - V_{DD} + I_{D2} R_{D2}$$

$$\Delta V_{out} = \Delta I_D R_D$$

$$\Delta V_{out} = G_m \Delta V_{in} R_D$$

Small signal differential voltage gain:

$$|A_v| = \frac{\Delta V_{out}}{\Delta V_{in}} = G_m R_D = \sqrt{\mu_n C_{ox} \frac{W}{L} \cdot I_{SS} \cdot R_D} \quad (6.13)$$

ΔV_{in1} is when $I_{D1} = I_{SS}$

$$\Delta V_{in1} = V_{GS1} - V_{TH1} \Rightarrow \Delta V_{in1} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

Voltage and Current Relationship:

$$I_{D1} - I_{D2} = \frac{\mu_n C_{ox} W}{2L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2} \quad (6.14)$$

Equation for Transconductance:

$$G_m = \frac{\mu_n C_{ox} W}{2L} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2\Delta V_{in}^2} \quad (6.15)$$

 


Figure 6.2: (a) Plot of Current vs. Differential Input Voltage, (b) Plot of Transconductance

[4]

[5]

[2]

6.5 Single-ended vs Differential Input Comparison Plot

 


Figure 6.3: In-Phase vs Out-of-Phase Plots of Simulated $V(vo)$

6.6 Python Code Listings

The Python code for differential pair analysis can be found in the Appendix (listing E.1).

6.7 Conclusion

The lab successfully demonstrated the behavior and advantages of a MOS differential pair, specifically highlighting its performance using the ALD1105 MOSFET array. Through both theoretical analysis and practical implementation, the lab emphasized the superiority of differential signaling over single-ended signaling in terms of noise rejection and signal integrity. The measured DC operating points closely matched simulation predictions, validating the circuit's proper biasing and symmetrical configuration.

AC analysis further confirmed the benefits of differential operation. The differential gain was significantly higher and more stable, while the common-mode gain was drastically reduced compared to the single-ended configuration. This led to a much higher common-mode rejection ratio (CMRR), both in simulation and measurement, for the differential output. The measured CMRR increased from 21.7 dB (single-ended) to 48.3 dB (differential), demonstrating the effectiveness of the differential pair in suppressing common-mode noise.

Theoretical derivations, supported by LTSpice simulations, aligned with experimental results, strengthening the understanding of current steering mechanisms and transconductance behavior in MOS differential amplifiers. In summary, the lab clearly illustrated the functional and practical benefits of differential signaling in analog circuit design, particularly in enhancing noise immunity and ensuring signal fidelity in mixed-signal environments.

References

- [1] Dwyer Omega. “Differential signal vs single-ended inputs”, Accessed: Mar. 31, 2025. [Online]. Available: <https://www.dwyeromega.com/en-us/resources/differential-or-single-ended>.
- [2] B. Razavi, *Single-ended and differential operation, basic differential pair, common-mode response, differential pair with mos loads*, Lecture notes.
- [3] S. Palermo. “Lab 6: Differential pair characterization”, Accessed: Mar. 31, 2025. [Online]. Available: <https://people.engr.tamu.edu/spalermo/ecen474/Lab6.pdf>.
- [4] H. Aboushady. “Differential amplifier and differential signaling: Lecture 10, ece315 / ece515”. Lecture slides, extensively used in project. [Online]. Available: <https://ece315.example.edu/lectures/lecture10>.
- [5] L. Rhodes. “What is the difference between single-ended and differential signals?”, Accessed: Mar. 31, 2025. [Online]. Available: <https://www.dynapar.com/faq/what-is-the-difference-between-single-ended-and-differential-signals>.

Chapter 7

Lab 7 — MOS Differential Pair: Current Mirror

7.1 Lab Assignment Goals

This lab investigated the MOS differential pair composed of transistors Q_1 and Q_2 with a current mirror load formed by Q_3 and Q_4 , functioning as a differential to single-ended amplifier stage. The common-mode rejection ratio (CMRR) was analyzed. The circuit was implemented using the ALD1105 MOSFET array. Differential operation was examined to evaluate its effectiveness in noise rejection and signal integrity. LTSpice simulations were performed to validate theoretical predictions and support measurement techniques.

 



Figure 7.1: The pin-out and block diagram of the ALD1105. **Note:** V^- is the body of the NMOS devices and is connected to the source, and V^+ is the body of the PMOS devices, which is also connected to its source.

7.2 Experiment 1: MOS Differential Pair DC Measurements

The MOS differential pair circuit was constructed on the Analog Discovery Studio as shown below:

- The resistance R_{CS} was measured and recorded.
- The DC operating point was determined by measuring node voltages and calculating the corresponding currents.

Common-Mode Input

 

$$V_{DD} = 12 \text{ V} \quad -V_{SS} = -12 \text{ V} \quad R_{CS} = 10 \text{ k} \Omega \quad V_{I1} = V_{I2} = 0 \text{ V}$$

Observations

The simulated values for the drain currents (I_D) based on node voltages (V_G and V_S) are all the same while measured values differ for the pairs formed by Q1 with Q2 and Q3 with Q4. Specifically:

- **Q1/Q2 (NMOS):** $I_D = 514.000 \mu\text{A}$ (simulated)
- **Q3/Q4 (PMOS):** $I_D = 514.000 \mu\text{A}$ (simulated)

Compared to the measured values:

- **Q1:** $663.487 \mu\text{A}$, **Q2:** $343.301 \mu\text{A}$ (measured)
- **Q3:** $663.487 \mu\text{A}$, **Q4:** $343.301 \mu\text{A}$ (measured)

Observations:

- The measured current for Q2 is lower than the simulated value. This discrepancy is likely due to the quadratic relationship between drain current and overdrive voltage (V_{ov}), which makes I_D highly sensitive to small changes in V_{ov} , λ is another likely candidate for as a cause behind this discrepancy [1].
- Although Q2 shares the same V_S and V_G as Q1, and also taking into consideration that I_{D3} and I_{D4} should mirror one another, this does not result in an identical measured current. However, the measured current for Q2 is significantly lower, suggesting device mismatch or the influence of channel-length modulation (Early effect) [2].

A MOS differential pair with a current mirror load is used to amplify differential signals while rejecting common-mode noise. This topology is foundational in analog integrated circuit design.

- **Structure:** Transistors Q_1 and Q_2 form the differential pair, and Q_3 , Q_4 implement the current mirror load [2].

$$I_{D1} = I_{D2} = \frac{I_{RCS}}{2}$$

when $V_{I1} = V_{I2}$.

- **Active Load Benefits:**

- Converts differential current to single-ended output [1].
- Increases gain vs resistive loads:

$$A_{v,d} \approx g_m \cdot R_{out} \quad \text{with } R_{out} \gg R_{resistive}$$

- Improves common-mode rejection ratio (CMRR):

$$\text{CMRR} = \left| \frac{A_d}{A_{cm}} \right|$$

- **Matching:**

- Requires $Q_1 = Q_2$ and $Q_3 = Q_4$ for optimal performance.
- Imbalances introduce input offset voltage:

$$V_{OS} = \frac{I \cdot \Delta R}{2}$$

- **Common-mode suppression:**

$$V_{D1} = V_{D2} \Rightarrow V_O = 0 \quad (\text{ideal})$$


Common-mode gain will approach zero as the impedance of R_{CS} increases [3].

7.3 Experiment 2: MOS Differential Pair AC Response

The differential and common-mode gains were determined using measurement techniques, and the common-mode rejection ratio (CMRR) was calculated. The output was taken from node v_O with respect to ground.

- The differential input was applied using two synchronized sinusoidal signals, equal in magnitude but opposite in phase.
- The common-mode input was created by applying the same synchronized signal to both terminals with appropriate biasing.
- Measured resistor values were used for AC analysis in LTSpice.
- Measured data was recorded in the following summary tables.

Difference-Mode Inputs

 

$$V_{DD} = 12 \text{ V} \quad -V_{SS} = -12 \text{ V} \quad R_{CS} = 10 \text{ k}\Omega \quad V_{I1} = V_{I2} = 0 \text{ V}$$

- The circuit utilizes a current mirror load, which allows differential-mode current doubling and suppresses common-mode currents, making it effective for single-ended output without sacrificing gain [2].
- The differential-mode gain for a current mirror loaded differential pair is approximated as:

$$A_{v,d} \approx \frac{2g_{m3}}{g_{o2} + g_{o4} + G_L}$$

where g_{m3} is the transconductance of the current mirror transistor, g_{o2}, g_{o4} are the output conductance, and G_L is the load conductance [2].

- In contrast, the common-mode gain is significantly smaller:

$$A_{v,cm} \approx \frac{g_{ob}}{2(g_{m2} + g_{o4} + G_L)}$$

This results in excellent rejection of common-mode noise, contributing to a high CMRR [2].

- From the small-signal model:

$$\text{CMRR} = \frac{A_{v,d}}{A_{v,cm}} \approx \frac{2g_{m3}}{g_{ob}} \cdot \frac{g_{m2}}{g_{o2} + g_{o4} + G_L}$$

High values of g_m and low output conductance are favorable for achieving high CMRR [2].

- The implementation also benefits from the mirrored topology which ensures that any common-mode signal appears equally at both inputs and is **effectively canceled out**, a principle demonstrated in both theoretical and experimental studies [4].
- According to [5], a finite output impedance in the tail current source slightly reduces CMRR due to common-mode to differential-mode conversion:

$$A_{cm} \approx \frac{1}{1 + 2g_m R_{SS}}$$

- (for this experiment, $R_{SS} = R_{CS}$)

where R_{SS} is the source degeneration resistance. Ideally, this should be large.

- The presence of mismatches (e.g., $g_{m1} \neq g_{m2}$) introduces additional differential components into the output in response to a purely common-mode input, reducing CMRR. This is quantified using:

$$A_{CM \rightarrow DM} \approx \frac{(g_{m1} - g_{m2})R_{SS}}{g_{m1} + g_{m2} + \dots}$$

which highlights the importance of symmetric layout and transistor matching [6].

- Overall, using a current mirror as an active load provides significant advantages in terms of:
 - Converting differential signal to single-ended output efficiently
 - Doubling the effective gain compared to resistive loads
 - Minimizing common-mode gain
 - Enabling high CMRR with compact layout

as emphasized in multiple foundational sources [1], [2], [6].

DC Operating Point				
Device	Quantity	Simulated	Measured	Units
Q_1	I_D	514.000	540.335	μA
	$ V_{OV} $	1.267	1.365	V
	V_G	0.000	0.000	V
	V_D	9.010	8.606	V
	V_S	-1.844	-1.985	V
Q_2	I_D	514.000	540.335	μA
	$ V_{OV} $	1.267	1.365	V
	V_G	0.000	0.000	V
	V_D	9.011	8.606	V
	V_S	-1.844	-1.985	V
Q_3	I_D	514.000	540.335	μA
	$ V_{OV} $	2.343	2.394	V
	V_G	9.010	8.606	V
	V_D	9.010	8.606	V
	V_S	12.000	12.000	V
Q_4	I_D	514.000	540.335	μA
	$ V_{OV} $	2.343	2.394	V
	V_G	9.010	8.606	V
	V_D	9.010	8.606	V
	V_S	12.000	12.000	V


Table 7.1: DC Summary Table

Quantity	Measured	Units
R_{CS}	9.872	$k\Omega$

Table 7.2: Resistor Summary

AC Summary - Single Ended			
Quantity	Simulated	Measured	Units
A_d	44.888	24.161	V/V
A_d	33.040	27.662	dB
A_{cm}	0.105	0.183	V/V
A_{cm}	-19.591	-14.751	dB
CMRR	52.632	42.413	dB

Table 7.3: AC Summary Table - Single Ended Output

 Figure 7.2: Differential Mode $V(vo)$

 


Figure 7.3: Common Mode V(vo)

7.4 Python Output: Simulated vs Measured % Difference

===== DC Percent Difference Table =====						
Dev	Quant	Sim	Meas	Unit	Diff	%Diff
Q1	ID	514.0	540.3	uA	26.3	5.116
Q1	VOV	1.267	1.365	V	0.098	7.733
Q1	VG	1.840	0.000	V	1.840	N/A
Q1	VD	10.900	8.606	V	2.294	21.038
Q1	VS	0.000	-1.985	V	1.985	N/A
Q2	ID	514.0	540.3	uA	26.3	5.116
Q2	VOV	1.267	1.365	V	0.098	7.733
Q2	VG	1.840	0.000	V	1.840	100.000
Q2	VD	10.900	8.606	V	2.294	21.038
Q2	VS	0.000	-1.985	V	1.985	N/A
Q3	ID	514.0	540.3	uA	26.3	5.116
Q3	VOV	2.343	2.394	V	0.051	2.177
Q3	VG	-2.990	8.606	V	11.596	388.125
Q3	VD	-2.990	8.606	V	11.596	388.125
Q3	VS	0.000	12.000	V	12.000	N/A
Q4	ID	514.0	540.3	uA	26.3	5.116
Q4	VOV	2.343	2.394	V	0.051	2.177
Q4	VG	-2.990	8.606	V	11.596	388.125
Q4	VD	-2.990	8.606	V	11.596	388.125
Q4	VS	0.000	12.000	V	12.000	N/A

7.5 Python Code Listings

The Python implementations for the current mirror analysis can be found in the Appendix: DC Summary Calculations (listing F.1), AC Summary Calculations (listing F.2), and Data Analysis and Plots (listing F.3).

7.6 Conclusion

This lab demonstrated the operation and advantages of a MOSFET differential pair using the ALD1105 IC. By constructing and analyzing the circuit both experimentally and through LT-Spice simulations, we verified that differential signaling offers significant benefits over single-ended approaches. Notably, the differential configuration achieved a much higher common-mode rejection ratio (CMRR), with simulated and measured values of approximately 59.9 dB and 48.3 dB respectively, compared to 17.1 dB and 21.7 dB for single-ended output. These results confirm the superior noise rejection capabilities inherent to differential systems. Theoretical modeling was reinforced by close agreement between simulated and measured values for

parameters such as differential gain and DC operating points. Overall, this lab emphasized the importance of differential signaling in high-fidelity analog design and the utility of simulation tools in predicting and optimizing circuit performance.

References

- [1] A. Rajesh and D. B. L. Raju, “Design of a differential amplifier using current mirror as active load”, *International Journal of Engineering Research and General Science*, vol. 2, no. 6, pp. 43–47, 2014, ISSN: 2091-2730.
- [2] C. Fonstad. “Two active loads for differential amplifiers: The lee load and the current mirror load”, Accessed: Apr. 4, 2025. [Online]. Available: https://ocw.mit.edu/courses/6-012-microelectronic-devices-and-circuits-fall-2009/27dce54a63b9a793be542cb457d1c865_MIT6_012F09_lec20_loads.pdf.
- [3] G. S. Deo, J. A. Totlani, K. E. Mamidi, and C. V. Mahamuni, “Performance analysis of bimos differential pair with active load, wilson and widlar current mirrors, and diode connected topology”, in *2020 4th International Conference on Intelligent Computing and Control Systems (ICICCS)*, Madurai, India: IEEE, 2020, pp. 99–104. DOI: 10.1109/ICICCS48265.2020.9121038.
- [4] B. Razavi, *Single-ended and differential operation, basic differential pair, common-mode response, differential pair with mos loads*, Lecture notes.
- [5] S. Palermo. “Lab 6: Differential pair characterization”, Accessed: Mar. 31, 2025. [Online]. Available: <https://people.engr.tamu.edu/spalermo/ecen474/Lab6.pdf>.
- [6] M. Shashmi. “Lecture 16: Cmos amplifiers”, Accessed: Apr. 4, 2025. [Online]. Available: https://www.iiitd.edu.in/~mshashmi/CMOS_2015/Lecture_Slides/Lect_16_2015.pdf.

Chapter 8

Lab 8 — VNA Measurement: De-Embedding S-Parameters

8.1 Lab Assignment Goals

This laboratory experiment focused on the fundamentals of using a Vector Network Analyzer (VNA) to characterize the frequency-domain behavior of high-frequency components and networks. The VNA served as a critical instrument for measuring complex scattering parameters (S -parameters), providing insight into how RF signals are reflected and transmitted through a device under test (DUT). These measurements are essential for understanding the behavior of RF circuits such as filters, amplifiers, and interconnects. [1]

A critical aspect of obtaining accurate S -parameter measurements is the de-embedding process. De-embedding mathematically removes the parasitic effects introduced by test fixtures, connectors, or interconnects that are not part of the actual DUT. Without proper de-embedding, the measured response would inaccurately represent the true behavior of the DUT, potentially leading to erroneous conclusions regarding device performance. [2]

In this experiment, the frequency response of both a low-pass filter (LPF) and a high-pass filter (HPF) was measured. The data were analyzed both in raw form and after de-embedding to observe how parasitic elements introduced by the measurement environment influenced the apparent performance. Resonant behaviors observed in the test setup were discussed, alongside corrective techniques based on network modeling. [3]

8.2 S-Parameter De-embedding Methods

S -parameter de-embedding was conducted according to industry standards, specifically adhering to principles outlined by the IEEE Standard for Test Procedures for High-Frequency Transmission Lines on Printed Boards [4]. The de-embedding methodology relied on characterizing and mathematically removing the contributions of the test environment using three standard measurements: Open, Short, and Thru structures.

8.3 Measurement Fixture and De-Embedding Theory

All fixtures will add their own frequency-dependent errors to a device under test. Generally, a DUT is measured while sandwiched between two coaxial test fixtures, and these fixtures are absolutely necessary in order to perform measurements, so this is unavoidable. [4] By modeling each fixture with an S -matrix (S_{FI} on the input side and S_{FO} on the output side) we can mathematically remove their influence via network transformations (Fig. 8.1).

 


Figure 8.1: Block-diagram representation of the measurement topology: the VNA observes the cascade of input fixture, DUT, and output fixture. [5]

For any two-port network the incident (a_1, a_2) and reflected (b_1, b_2) traveling waves are related through the scattering matrix (Fig. 8.2):

$$\begin{pmatrix} b_1 & b_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} & S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 & a_2 \end{pmatrix}. \quad (8.1)$$

 


Figure 8.2: Directionality of the four scattering parameters for a reciprocal two-port. [5]

Because S -parameters do not cascade directly, they are converted to chain (ABCD) or transmission (T) parameters (Fig. 8.3):

$$T_{11} = -\frac{S_{11}S_{22} - S_{12}S_{21}}{S_{21}}, \quad T_{12} = \frac{S_{11}}{S_{21}}, \quad T_{21} = -\frac{S_{22}}{S_{21}}, \quad T_{22} = \frac{1}{S_{21}}. \quad (8.2)$$

 


Figure 8.3: Formulae for converting S -parameters to T -parameters. [5]

After conversion, the DUT's transmission matrix is extracted by left-and right-multiplying the cascade with the inverses of the fixture matrices:

$$T_{\text{DUT}} = T_{FI}^{-1} \cdot [T_{FI} + T_{DUT} + T_{FO}] \cdot T_{FO}^{-1} \quad (8.3)$$

Finally, the corrected S -parameters are recovered by back-transforming (Fig. 8.4):

$$S_{21} = \frac{1}{T_{22}}, \quad S_{11} = \frac{T_{12}}{T_{22}}, \quad S_{22} = -\frac{T_{21}}{T_{22}}, \quad S_{12} = \frac{T_{11}T_{22} - T_{12}T_{21}}{T_{22}}. \quad (8.4)$$

 


Figure 8.4: Conversion of T -parameters back to S -parameters once fixture effects are removed. [5]

8.3.1 Open, Short, and Thru Measurements

Open (Open . s2p), Short (Short . s2p), and Thru (Thru . s2p) calibration standards were first measured. These structures provided the necessary data to model the parasitic admittance and impedance of the fixture environment.

The Open measurement captured the parasitic capacitive effects present when the DUT port was left unconnected. The Short measurement captured the parasitic inductive effects of a direct short-circuit at the measurement plane. Finally, the Thru measurement provided a baseline transmission path between ports without a DUT, capturing the insertion loss and phase delay of the interconnect alone.

Using these three standards, error correction terms were extracted, allowing the fixture contributions to be subtracted from the raw DUT measurements.

8.3.2 Low-Pass Filter De-embedding

The de-embedding process for the low-pass filter began by measuring the raw S -parameters of the DUT. Fixture parasitics were removed by applying a de-embedding algorithm that utilized the Open, Short, and Thru standard measurements. The transmission (S_{21}) and reflection (S_{11}) parameters were evaluated before and after de-embedding. [6]

The raw measurements exhibited parasitic-induced distortions, particularly in the stop-band region where fixture resonances introduced artificial dips. [7] After de-embedding, the measured response revealed the true low-pass behavior with the expected cutoff characteristics and improved stop-band rejection.

Low-Pass Filter Results

 


Figure 8.5: Comparison of LPF S -parameter measurements before and after de-embedding using OST method.

8.3.3 High-Pass Filter De-embedding

For the high-pass filter, the same de-embedding approach was applied. Raw measurements showed a low-frequency insertion loss which is caused by the parasitic effects of the measurement from the fixtures themselves interacting with the device under test. De-embedding corrected the transmission and reflection measurements by accounting for these parasitic effects.

The corrected S_{21} data exhibited a sharper roll-off at low frequencies, consistent with the expected high-pass behavior. Reflections measured through S_{11} similarly demonstrated improved impedance matching post-de-embedding, confirming the effectiveness of the de-embedding process.

8.4 Experimental Results and Analysis

8.4.1 High-Pass Filter Results

 


Figure 8.6: Comparison of HPF S -parameter measurements before and after de-embedding using OST method.

8.4.2 Verification with Keysight ADS Simulations

To cross-validate the bench measurements and Python-based de-embedding, each calibration structure and DUT was re-created in *Keysight ADS*. The built-in `De_Embed2` element was configured for an *Open–Short–Thru* (OST) strategy (Fig.8.7). The same touchstone files captured on the VNA were used as stimulus, ensuring that any disparity between environments was attributable to algorithmic differences rather than data capture.

Keysight ADS Work-Flow

1. Import `Open.s2p`, `sparam_files/Short.s2p`, and `sparam_files/Thru.s2p` into ADS as two-port S-parameter blocks.
2. Cascade the inverse fixture model (`De_Embed2`) on both ports surrounding the DUT, mirroring the physical setup (left-reference configuration; see Fig. 8.9).
3. Sweep 1 MHz–60 MHz with a 118 kHz step (matching the bench sweep).
4. Export post-de-embedding data as `sparam_files/LPF_OST_De_Embedded.s2p` for direct overlay against Python results.

Low-Pass Filter

Figure 8.10 overlays the ADS-derived response on top of the Python workflow. The traces are indistinguishable within 0.02 dB across the pass-band and stop-band, validating both approaches. Minor ripple near 15 MHz is present in both environments, confirming it is a genuine attribute of the filter rather than fixture error.

Fixture-Only Structures

The standalone “open” and “short” files were also de-embedded to sanity-check the algorithm. As expected, the open shows a near-zero dB through with a capacitive reflection arc on the Smith chart, whereas the short produces the complementary inductive arc with reverse isolation at 3.5 MHz (Fig. 8.11).

 


Figure 8.7: Plot generated by python code implementing the IEEE thru de-embedding standard. [4]

De-embed "Short-Open-Thru" LPF Data

 


Figure 8.8: ADS schematic implementing OST de-embedding with De_EMBED2. The DUT is the central LPF touchstone block.

 


Figure 8.9: Left-reference positioning used in the ADS De_Embed2 element.

LPF - "SHORT-OPEN-THRU" De-Embedded S-Parameters vs. Frequency

 


Figure 8.10: Low-pass filter after OST de-embedding: ADS simulation. Compare with Fig. 8.5.

 


Figure 8.11: Validation of de-embedding on fixture structures.


The previously un-recognizable curve a low-pass filter response appears after S -parameter de-embedding (top). Approaching its resonant frequency, the short fixture $S_{(1,2)}$ measurement demonstrates a large peak around 4 MHz, which indicates a large amount of inductance present in the DUT measured data (bottom).

8.5 Python Code Listings

The Python code for S-parameter de-embedding can be found in the Appendix: LPF Open-Short-Thru Method (listing G.1), Thru Method (listing G.2), LPF IEEE Thru Method (listing G.3), 2x Thru Method (listing G.4), HPF OST Method (listing G.5), and HPF IEEE Thru Method (listing G.6).

 8.6 Conclusion

- Practical experience was gained in the setup and calibration of a Vector Network Analyzer (VNA), including the application of Short-Open-Load-Thru (SOLT) calibration standards.
- The physical significance of scattering parameters, particularly S_{21} (forward transmission) and S_{11} (input reflection), was investigated and analyzed.
- The frequency responses of low-pass and high-pass filters were measured, with key characteristics such as cutoff frequencies and stop-band attenuation identified.
- Industry-standard de-embedding techniques were applied to isolate the intrinsic behavior of the device under test (DUT) from parasitic effects introduced by the measurement fixtures.
- The effects of de-embedding on the measured data were analyzed to highlight the importance of fixture error correction in high-frequency characterization.
- Best practices in RF measurement procedures were reinforced, and the practical application of network theory concepts was demonstrated through experimental verification.



References

- [1] *Ieee standard for test procedures for high-frequency transmission lines on printed boards*, 2011.
- [2] N. Liu et al., “Experimental characterization of the effect of metal dummy fills on spiral inductors”, in *2007 IEEE Radio Frequency Integrated Circuits (RFIC) Symposium*, 2007, pp. 307–310. DOI: 10.1109/RFIC.2007.380889.
- [3] S. Amakawa, K. Katayama, K. Takano, T. Yoshida, and M. Fujishima, “Comparative analysis of on-chip transmission line de-embedding techniques”, in *2015 IEEE International Symposium on Radio-Frequency Integration Technology (RFIT)*, 2015, pp. 91–93. DOI: 10.1109/RFIT.2015.7377897.
- [4] IEEE, *Ieee standard for electrical characterization of printed circuit board and related interconnects*, Accessed: 2025-04-19, 2020.
- [5] Test & Measurement Tips. “What is de-embedding and how do i perform it (part 1)?”, Accessed: Apr. 19, 2025. [Online]. Available: <https://www.testandmeasurementtips.com/what-is-de-embedding-and-how-do-i-perform-it-part-1/>.
- [6] S.-J. Moon, X. Ye, and R. Smith, “Comparison of trl calibration vs. 2x thru de-embedding methods”, in *2015 IEEE Symposium on Electromagnetic Compatibility and Signal Integrity*, 2015, pp. 176–180. DOI: 10.1109/EMCSI.2015.7107681.
- [7] S.-Y. Tang, X.-C. Wei, and D. Wang, “A novel de-embedding method based on artificial neural network”, in *2024 International Symposium on Electromagnetic Compatibility – EMC Europe*, 2024, pp. 925–930. DOI: 10.1109/EMCEurope59828.2024.10722350.

Appendix A

Appendix

Appendix A

Python Code Listings for Lab 01

Code Listing A.1: Lab 01: Experiment 1: NMOS Sweep

```
1 import serial
2 import time
3 import numpy as np
4 import pandas as pd
5 import matplotlib.pyplot as plt
6
7 # Serial Configuration
8 serial_port = 'COM4' # Verify the COM port
9 baud_rate = 9600
10 timeout = 1
11 ngu = serial.Serial(port=serial_port, baudrate=baud_rate, timeout=
    ↪ timeout)
12
13 # Sweep Parameters
14 start_voltage = 0 # Starting VDS (V)
15 end_voltage = 8 # Ending VDS (V)
16 step_voltage = 0.1 # Step size (100mV)
17 sweep_voltages = np.arange(start_voltage, end_voltage + step_voltage
    ↪ , step_voltage)
18
19 # Data Storage
20 all_data = {}
21
22 try:
23     # Reset the instrument to a safe state
24     ngu.write(b'*RST\n')
25     time.sleep(0.5) # Allow some time for the reset to complete
26
27     # Set initial voltage and current limits to safe values
28     ngu.write(b'SOUR:VOLT 0\n') # Set voltage to 0 V
29     ngu.write(b'SOUR:CURREN 0.02\n') # Set current limit to 20 mA
30     ngu.write(b'SENS:CURREN:RANG:AUTO ON\n') # Set current range to
    ↪ Auto
31     time.sleep(0.1)
32
```



```

33 # Enable the output
34 ngu.write(b'OUTP ON\n')
35 time.sleep(0.1)
36
37 while True:
38     # Prompt for VGS from the user in the Python Console
39     try:
40         vgs = float(input("Enter VGS value (or type 'stop' to
41                             ↪ exit): "))
42     except ValueError:
43         print("Stopping sweeps.")
44         break
45
46     print(f"Starting sweep for VGS = {vgs} V")
47
48     # Initialize lists for this sweep
49     measured_voltages = []
50     currents = []
51
52     # This step resets the voltage back to 0 before a new sweep
53     ↪ begins
54     ngu.write(b'SOUR:VOLT 0\n')
55     time.sleep(0.5) # Pause to ensure voltage is set before the
56     ↪ next sweep
57
58     for voltage in sweep_voltages:
59         # Set VDS (controlled by NGU401)
60         ngu.write(f'SOUR:VOLT {voltage:.3f}\n'.encode())
61         time.sleep(0.3) # The time inbetween sweep points
62
63         # Measure current
64         ngu.write(b'MEAS:CURR?\n')
65         measured_current = float(ngu.readline().decode().strip()
66                                 ↪ )
67         currents.append(measured_current)
68
69         # Measure voltage
70         ngu.write(b'MEAS:VOLT?\n') # SCPI command to measure
71         ↪ voltage
72         measured_voltage = float(ngu.readline().decode().strip()
73                                 ↪ )
74         measured_voltages.append(measured_voltage)
75
76         # Print progress
77         print(f"VGS: {vgs:.2f} V, VDS: {measured_voltage:.3f} V,
78               ↪ Measured Current: {measured_current:.6f} A")
79
80     # Save this sweep's data_vds in the dictionary
81     all_data[f'VGS={vgs:.2f}V'] = {'VDS': measured_voltages, '
82     ↪ Current': currents}

```

```

76     # Disable output after all sweeps
77     ngu.write(b'OUTP OFF\n')
78
79 except Exception as e:
80     print(f"An error occurred: {e}")
81 finally:
82     ngu.close() # This closes communication with the instrument
83
84     # Plot all data_vds collected
85     plt.figure()
86     for vgs_label, data in all_data.items():
87         plt.plot(data['VDS'], data['Current']*1e3, label=f"VGS = {
            ↪ vgs_label}") # Scaling current to mA
88
89     plt.xlabel("$V_{DS}$ (V)")
90     plt.ylabel("$I_{D}$ (mA)")
91     plt.title("Experiment 1 - $I_{D}$ vs. $V_{DS}$")
92     plt.legend()
93     plt.grid(True)
94     plt.show()
95
96     # Prepare MultiIndex DataFrame
97     multi_index_columns = []
98     multi_index_data = []
99
100    for vgs_label, data in all_data.items():
101        multi_index_columns.extend([(vgs_label, 'VDS'), (vgs_label,
            ↪ 'Current')])
102        multi_index_data.append(data['VDS'])
103        multi_index_data.append(data['Current'])
104
105    # Convert to DataFrame
106    multi_index = pd.MultiIndex.from_tuples(multi_index_columns,
            ↪ names=['VGS', 'Parameter'])
107    formatted_data = pd.DataFrame(np.array(multi_index_data).T,
            ↪ columns=multi_index)
108
109    # Save to CSV
110    output_file = 'NMOS_Parametric_Sweep.csv'
111    formatted_data.to_csv(output_file, index=False)
112    print(f"All sweeps completed. Data saved to '{output_file}'.")

```

Code Listing A.2: Lab 01: Experiment 2: V_{GS} Sweep

```

1 import serial
2 import pyvisa
3 import time
4 import numpy as np
5 import pandas as pd
6 import matplotlib.pyplot as plt
7
8 # Serial Configuration
9 serial_port = 'COM4' # Verify the COM port
10 baud_rate = 9600
11 timeout = 1
12 ngu = serial.Serial(port=serial_port, baudrate=baud_rate, timeout=
    ↪ timeout)
13
14 # Initialize VISA Resource Manager for the DMM
15 rm = pyvisa.ResourceManager()
16
17 dmm = rm.open_resource('USB0::0x05E6::0x6500::04499374::INSTR') #
    ↪ Name of instrument
18 dmm.write("*RST") # Resets instrument
19 dmm.write('SENS:FUNC "CURR:DC"') # Set DC current measurements
20 dmm.write('SENS:CURR:RANG:AUTO ON') # Enables auto ranging
21
22 # Sweep Parameters
23 start_voltage = 0 # Starting VGS (V)
24 end_voltage = 4 # Ending VGS (V)
25 step_voltage = 0.1 # Step size (200mV)
26 sweep_voltages = np.arange(start_voltage, end_voltage + step_voltage
    ↪ , step_voltage)
27
28 # Data Storage
29 all_data = {}
30
31 try:
32     # Reset the instrument to a safe state
33     ngu.write(b'*RST\n')
34     time.sleep(0.5) # Allow some time for the reset to complete
35
36     # Set initial voltage and current limits to safe values
37     ngu.write(b'SOUR:VOLT 0\n') # Set voltage to 0 V
38     ngu.write(b'SOUR:CURR 0.02\n') # Set current limit to 20 mA
39     ngu.write(b'SENS:CURR:RANG:AUTO ON\n') # Set current range to
        ↪ Auto
40     time.sleep(0.1)
41
42     # Enable the output
43     ngu.write(b'OUTP ON\n')
44     time.sleep(0.1)
45
46 while True:

```

```

47     # Prompt for VDS
48     try:
49         vds = float(input("Enter VDS value (or type 'stop' to
           ↪ exit): "))
50     except ValueError:
51         print("Stopping sweeps.")
52         break
53
54     print(f"Starting sweep for VDS = {vds} V")
55
56     # Initialize lists for this sweep
57     measured_voltages = []
58     currents = []
59
60     # This step resets the voltage back to 0 before a new sweep
           ↪ begins
61     ngu.write(b'SOUR:VOLT 0\n')
62     time.sleep(0.5) # Pause to ensure voltage is set before the
           ↪ next sweep
63
64     for voltage in sweep_voltages:
65         # Set VGS (controlled by NGU401)
66         ngu.write(f'SOUR:VOLT {voltage:.3f}\n'.encode())
67         time.sleep(0.3)
68
69         # Measure voltage
70         ngu.write(b'MEAS:VOLT?\n') # SCPI command to measure
           ↪ voltage
71         measured_voltage = float(ngu.readline().decode().strip()
           ↪ )
72         measured_voltages.append(measured_voltage)
73
74         # Measure current through sense ports
75         try:
76             dmm_current = float(dmm.query("MEAS:CURREN:DC?").strip()
           ↪ ())
77             currents.append(dmm_current)
78         except Exception as e:
79             print(f"Error querying current from DMM: {e}")
80             currents.append(None) # Append None for failed
           ↪ measurement to keep data_vds consistent
81
82         time.sleep(0.2) # Small delay for DMM to process
           ↪ commands
83
84         # Print progress
85         print(f"VDS: {vds:.2f} V, VGS: {measured_voltage:.3f} V,
           ↪ Measured Current: {dmm_current if 'dmm_current' in
           ↪ locals() else 'N/A'} A")
86
87

```

```

88     # Save this sweep's data_vds in the dictionary
89     all_data[f'VDS={vds:.2f}V'] = {'VGS': measured_voltages, '
    ↪ Current': currents}
90
91     # Disable output of NGU after all sweeps
92     ngu.write(b'OUTP OFF\n')
93
94 except Exception as e:
95     print(f"An error occurred: {e}")
96 finally:
97     ngu.close()
98     dmm.close()
99
100    # Plot all data_vds collected
101    plt.figure()
102    for vds_label, data in all_data.items():
103        plt.plot(data['VGS'], data['Current']*1e3, label=f"VDS = {
    ↪ vds_label}") # Plot in mA
104
105    plt.xlabel("$V_{GS}$ (V)")
106    plt.ylabel("$I_{D}$ (mA)")
107    plt.title("Experiment 2 - $I_{D}$ vs. $V_{GS}$")
108    plt.legend()
109    plt.grid(True)
110    plt.show()
111    plot_filename = 'NMOS_VGS_IV_Curve.png' # You can change the
    ↪ file name and format as needed
112    plt.savefig(plot_filename, dpi=300)
113
114    # Prepare MultiIndex DataFrame
115    multi_index_columns = []
116    multi_index_data = []
117
118    for vds_label, data in all_data.items():
119        multi_index_columns.extend([(vds_label, 'VGS'), (vds_label,
    ↪ 'Current')])
120        multi_index_data.append(data['VGS'])
121        multi_index_data.append(data['Current'])
122
123    # Convert to DataFrame
124    multi_index = pd.MultiIndex.from_tuples(multi_index_columns,
    ↪ names=['VDS', 'Parameter'])
125    formatted_data = pd.DataFrame(np.array(multi_index_data).T,
    ↪ columns=multi_index)
126
127    # Save to CSV
128    output_file = 'VGS_NMOS_Parametric_Sweep.csv'
129    formatted_data.to_csv(output_file, index=False)
130    print(f"All sweeps completed. Data saved to '{output_file}'.")

```

Code Listing A.3: Lab 01: Data Analysis

```

1 import pandas as pd
2 import numpy as np
3 import matplotlib.pyplot as plt
4
5 # Load the CSV file for ID vs. VDS family of curves
6 file_path_vds = 'NMOS_Parametric_Sweep.csv'
7 data_vds = pd.read_csv(file_path_vds)
8
9 # Load the CSV file for ID vs. VGS family of curves
10 file_path_vgs = 'VGS_NMOS_Parametric_Sweep.csv'
11 data_vgs = pd.read_csv(file_path_vgs)
12
13 # Prepare dictionaries to store data_vds by VGS and data_vgs by VDS
14 all_data_vds = {}
15 all_data_vgs = {}
16
17 for col in data_vds.columns:
18     if 'VGS=' in col and '.1' not in col:
19         vgs_label = float(col.split('=')[1].replace('V', '')) #
20         ↪ Extract numerical VGS value
21         vds = pd.to_numeric(data_vds[col], errors='coerce').dropna()
22         ↪ .values
23         current_vds = pd.to_numeric(data_vds[f"{col}.1"], errors='
24         ↪ coerce').dropna().values
25         all_data_vds[vgs_label] = {'VDS': vds, 'Current':
26         ↪ current_vds}
27
28 for col in data_vgs.columns:
29     if 'VDS=' in col and '.1' not in col:
30         vds_label = float(col.split('=')[1].replace('V', '')) #
31         ↪ Extract numerical VDS value
32         vgs = pd.to_numeric(data_vgs[col], errors='coerce').dropna()
33         ↪ .values
34         current_vgs = pd.to_numeric(data_vgs[f"{col}.1"], errors='
35         ↪ coerce').dropna().values
36         all_data_vgs[vds_label] = {'VGS': vgs, 'Current':
37         ↪ current_vgs}
38
39 # Create subplots (2 rows, 2 columns)
40 fig, axs = plt.subplots(2, 2, figsize=(16, 12))
41 fig.suptitle('NMOS Characterization and Analysis', fontsize=18)
42
43 # Plot ID vs. VDS data (top left)
44 for vgs_label, data_vds in all_data_vds.items():
45     axs[0, 0].scatter(data_vds['VDS'], data_vds['Current'] * 1e3,
46         ↪ label=f"$V_{{GS}}$ = {vgs_label:.1f}")
47     axs[0, 0].set_title('$I_{{D}}$ vs. $V_{{DS}}$ Curves')
48     axs[0, 0].set_xlabel('$V_{{DS}}$ (V)')
49     axs[0, 0].set_ylabel('$I_{{D}}$ (mA)')
50     axs[0, 0].legend()

```

```

42  axs[0, 0].grid(True)
43
44  # Plot ID vs. VGS data (top right)
45  for vds_label, data_vgs in all_data_vgs.items():
46      axs[0, 1].scatter(data_vgs['VGS'], data_vgs['Current'] * 1e3,
47          ↪ label=f"$V_{{DS}}$ = {vds_label:.1f}")
48  axs[0, 1].set_title('$I_{{D}}$ vs. $V_{{GS}}$ Curves')
49  axs[0, 1].set_xlabel('$V_{{GS}}$ (V)')
50  axs[0, 1].set_ylabel('$I_{{D}}$ (mA)')
51  axs[0, 1].legend()
52  axs[0, 1].grid(True)
53
54  # Analyze sqrt(ID) vs. VGS (bottom right)
55  kn_values = []
56  vth_values = []
57  r2_values = []
58
59  for vds_label, data_vgs in all_data_vgs.items():
60      sqrt_id = np.sqrt(np.maximum(data_vgs['Current'], 0))
61      mask = (data_vgs['VGS'] >= 2.0) & (data_vgs['VGS'] <= 3.0) #
62          ↪ Linear region
63
64      # Perform linear fit
65      fit_params = np.polyfit(data_vgs['VGS'][mask], sqrt_id[mask], 1)
66      kn = (fit_params[0] ** 2) * 1e6 #  $\mu\text{A}/\text{V}^2$ 
67      vth = -fit_params[1] / fit_params[0]
68      kn_values.append(kn)
69      vth_values.append(vth)
70
71      # Calculate R^2 value
72      y_pred = np.polyval(fit_params, data_vgs['VGS'][mask])
73      r2 = 1 - np.sum((sqrt_id[mask] - y_pred) ** 2) / np.sum((sqrt_id
74          ↪ [mask] - np.mean(sqrt_id[mask])) ** 2)
75      r2_values.append(r2)
76
77      # Plot data points
78      axs[1, 1].scatter(data_vgs['VGS'][mask], sqrt_id[mask], label=f"
79          ↪ $V_{{DS}}$ = {vds_label:.1f}", alpha=0.7)
80
81      # Plot linear fit
82      axs[1, 1].plot(
83          data_vgs['VGS'][mask],
84          y_pred,
85          linestyle='--',
86          label=f"Fit $V_{{DS}}$ = {vds_label:.1f}"
87      )
88
89  # Calculate mean and standard deviation of parameters
90  kn_mean, kn_std = np.mean(kn_values), np.std(kn_values)

```

```

89 vth_mean, vth_std = np.mean(vth_values), np.std(vth_values)
90 r2_mean = np.mean(r2_values)
91
92 # Annotate the subplot with results
93 axs[1, 1].text(
94     0.5, 0.1,
95     f"$K_N$: {kn_mean:.2f} ± {kn_std:.2f} μA/V²\n"
96     f"$V_{TH}$: {vth_mean:.3f} ± {vth_std:.3f} V\n"
97     f"$R^{{2}}$: {r2_mean:.4f}",
98     transform=axs[1, 1].transAxes,
99     fontsize=12,
100     ha='center',
101     bbox=dict(facecolor='white', edgecolor='black')
102 )
103
104 # Finalize the plot
105 axs[1, 1].set_title(r'$\sqrt{I_{D}}$ vs. $V_{GS}$ with Linear Fits')
106 axs[1, 1].set_xlabel('$V_{GS}$ (V)')
107 axs[1, 1].set_ylabel(r'$\sqrt{I_{D}}$ (A$^{1/2}$)')
108 axs[1, 1].legend(loc='upper left')
109 axs[1, 1].grid(True)
110
111 # Analyze ID vs. VDS for VA (bottom left)
112 va_values = []
113
114 # Plot ID vs VDS and the linear fits for V_A calculation
115 for vgs_label, data_vds in all_data_vds.items():
116     # Filter the data based on the linear range: VDS >= VGS -
117     #   ↳ VTH_mean and VDS <= 8V
118     linear_mask = (data_vds['VDS'] >= vgs_label - vth_mean) & (
119         ↳ data_vds['VDS'] <= 8.0)
120     vds_linear = data_vds['VDS'][linear_mask]
121     id_linear = data_vds['Current'][linear_mask] * 1e3 # Scale
122         ↳ current to mA
123
124     # Perform linear fit
125     fit_params = np.polyfit(vds_linear, id_linear, 1) # Linear fit
126     va = -fit_params[1] / fit_params[0] # X-intercept (V_A)
127     va_values.append(va)
128
129     # Plot the data points and linear fit
130     axs[1, 0].scatter(vds_linear, id_linear, label=f"$V_{GS}$ = {
131         ↳ vgs_label:.1f}", s=20)
132     axs[1, 0].plot(
133         vds_linear,
134         np.polyval(fit_params, vds_linear),
135         linestyle="--",
136         label=f"Fit ($V_{GS}$ = {vgs_label:.1f})",
137     )
138
139 # Format the bottom-left subplot

```

```

136 axs[1, 0].set_title("$I_{D}$ vs. $V_{DS}$ with Linear Fits")
137 axs[1, 0].set_xlabel("$V_{DS}$ (V)")
138 axs[1, 0].set_ylabel("$I_{D}$ (mA)")
139 axs[1, 0].legend(fontsize=8)
140 axs[1, 0].grid(True)
141 # Annotate the subplot with individual VA results
142 va_text = "\n".join([f"$V_{{GS}}$={vgs_label:.1f}: $V_A$ = {va:.2f}
    ↪ V" for vgs_label, va in zip(all_data_vds.keys(), va_values)])
143 axs[1, 0].text(
144     0.5, 0.2,
145     va_text,
146     transform=axs[1, 0].transAxes,
147     fontsize=10,
148     ha='center',
149     bbox=dict(facecolor='white', edgecolor='black')
150 )
151
152
153 axs[1, 0].set_title('$V_A$ Analysis')
154 axs[1, 0].set_xlabel('$V_{DS}$ (V)')
155 axs[1, 0].set_ylabel('$I_{D}$ (mA)')
156 axs[1, 0].legend()
157 axs[1, 0].grid(True)
158
159 # Adjust layout and save
160 plt.tight_layout()
161 plt.savefig('NMOS_Characterization_Analysis.png', dpi=300)
162 plt.show()

```

Appendix B

Python Code Listings for Lab 02

Code Listing B.1: Lab 2: Experiment 1: Plot Measured vs Simulated Data

```
1 import ltspice
2 import numpy as np
3 import pandas as pd
4 import matplotlib.pyplot as plt
5
6 raw_file = "Lab_02_Exp_01A_Sim_NMOS_SWEEP_MEAS.raw"
7 file_path = "Experiment_1_Part_A_NMOS_Sweep_data.csv"
8
9 df = pd.read_excel(file_path)
10 print(df.head())
11
12 Mes_I_DF = pd.read_excel(file_path, usecols=["VGS=0.00V.1"])
13 Mes_I_uT = array = np.array(Mes_I_DF)
14 Mes_I = np.delete(Mes_I_uT, 0, axis=0)
15 Mes_VDs_DF = pd.read_excel(file_path, usecols=["VGS=0.00V"])
16 Mes_VDs_uT = array = np.array(Mes_VDs_DF)
17 Mes_VDs = np.delete(Mes_VDs_uT, 0, axis=0)
18
19 l = ltspice.Ltspice(raw_file)
20 l.parse()
21
22 signals = l.variables
23 print("Available signals:", signals)
24 Ird = l.get_data('I(Rd)')
25 voltageIN = l.get_data('V(vdd)')
26
27 plt.plot(voltageIN, Ird, label="Simulated Current", color="g", linestyle="-"
28         ↪ , linewidth=2)
29 plt.plot(Mes_VDs, Mes_I, label="Messured Current", color="r", linestyle="-"
30         ↪ , linewidth=2)
31 plt.xlabel('Voltage (V)')
32 plt.ylabel('Currnet (A)')
33 plt.title('Measured vs Simulation')
34 plt.legend()
35 plt.grid()
36 plt.show()
```

Code Listing B.2: Lab 2: Experiment 1: Extract OP Values from LTSpice Log File

```

1 # Path to the .log file
2 log_file_path = r'Labs/Lab-02/Lab_02_Exp_01_Sim_NMOS_SWEEP_OP.log'
3
4 # Function to extract values from the .log file
5 def extract_op_values_from_log(file_path):
6     results = {"VGS": None, "VDS": None, "ID": None, "VOV": None, "VTH":
7         ↪ None, "RD": None}
8     try:
9         with open(file_path, "r") as file:
10             lines = file.readlines()
11             for line in lines:
12                 # Search for Vgs, Vds, Id, Vth, and other relevant values
13                 if "Vgs:" in line:
14                     results["VGS"] = float(line.split()[1]) # Extract
15                     ↪ second value in the line
16                 elif "Vds:" in line:
17                     results["VDS"] = float(line.split()[1])
18                 elif "Id:" in line:
19                     results["ID"] = float(line.split()[1]) * 1e6 # Convert
20                     ↪ to µA
21                 elif "Vth:" in line:
22                     results["VTH"] = float(line.split()[1])
23                 elif "Vdsat:" in line:
24                     results["VOV"] = results["VGS"] - results["VTH"] #
25                     ↪ Calculate VOV if VGS and VTH are available
26     except Exception as e:
27         print(f"Error reading the .log file: {e}")
28     return results
29
30 # Call the function to extract values
31 op_values = extract_op_values_from_log(log_file_path)
32
33 # Display the extracted values
34 print("Extracted values from the .log file:")
35 for key, value in op_values.items():
36     if value is not None:
37         print(f"{key}: {value}")
38     elif key == "RD": # Ensuring RD is also printed
39         print(f"{key}: {value if value != 'Not found' else 'N/A'}")
40
41 import chardet
42 import pandas as pd
43 import os
44
45 log_file_path = r'Lab_02_Exp_01_Sim_NMOS_SWEEP_OP.log'
46
47 def extract_op_values_from_log(file_path):
48     results = {"VGS": None, "VDS": None, "ID": None, "VOV": None, "VTH":
49         ↪ None}
50     try:
51         # Detect file encoding dynamically
52         with open(file_path, 'rb') as file:
53             raw_data = file.read()
54             detected_encoding = chardet.detect(raw_data)['encoding']

```

```

52     # Read the file with the detected encoding
53     with open(file_path, "r", encoding=detected_encoding) as file:
54         lines = file.readlines()
55         for line in lines:
56             line = line.strip()
57
58             # Skip lines with "0.00e+00"
59             if "0.00e+00" in line:
60                 continue
61
62             if line: # Only process non-empty lines
63                 if "Vgs:" in line:
64                     results["VGS"] = float(line.split(":")[1].strip())
65                 elif "Vds:" in line:
66                     results["VDS"] = float(line.split(":")[1].strip())
67                 elif "Id:" in line and "device_current" not in line:
68                     results["ID"] = float(line.split(":")[1].strip())
69                     ↪ # Leave as is for CSV
70                 elif "Vth:" in line:
71                     results["VTH"] = float(line.split(":")[1].strip())
72                 elif "I(Rd):" in line:
73                     results["I(Rd)"] = float(line.split(":")[1].strip())
74                     ↪ )
75
76             # Calculate VOV (Overdrive Voltage)
77             if results["VGS"] is not None and results["VTH"] is not None:
78                 results["VOV"] = results["VGS"] - results["VTH"]
79
80 except Exception as e:
81     print(f"Error reading the .log file: {e}")
82
83 # Replace None with "Not found"
84 for key in results:
85     if results[key] is None:
86         results[key] = "Not found"
87
88 # Save the results to a CSV file
89 try:
90     save_path = os.path.dirname(file_path)
91     csv_file_path = os.path.join(save_path, "
92         ↪ Lab_02_Exp_01B_Sim_NMOS_SWEEP_OP.csv")
93
94     results_df = pd.DataFrame([results])
95     results_df.to_csv(csv_file_path, index=False)
96     print(f"CSV successfully saved to {csv_file_path}")
97 except Exception as e:
98     print(f"Error saving CSV file: {e}")
99
100 return results
101
102 def format_with_si_units(value, unit=""):
103     """
104     Format a numerical value with SI prefixes for better readability.
105     """
106     if isinstance(value, str): # Handle cases where the value is "Not
107         ↪ found"
108         return value

```

```

106     if unit == "A": # Handle current (amps) specifically
107         if abs(value) >= 1: # Value is in amperes
108             return f"{value:.2f} A"
109         elif abs(value) >= 1e-3: # Value is in milliamps
110             return f"{value * 1e3:.2f} mA"
111         elif abs(value) >= 1e-6: # Value is in microamps
112             return f"{value * 1e6:.2f}  $\mu$ A"
113         else: # Value is in nanoamps
114             return f"{value * 1e9:.2f} nA"
115     elif unit == "V": # Handle voltage
116         if abs(value) >= 1: # Value is in volts
117             return f"{value:.2f} V"
118         elif abs(value) >= 1e-3: # Value is in millivolts
119             return f"{value * 1e3:.2f} mV"
120         elif abs(value) >= 1e-6: # Value is in microvolts
121             return f"{value * 1e6:.2f}  $\mu$ V"
122     return f"{value:.2e} {unit}" # Default scientific notation with unit
123
124
125 # Test the function
126 op_values = extract_op_values_from_log(log_file_path)
127
128 # Print the results with proper SI units
129 print("\nSimulated values from the LTSpice .log file:")
130 for key, value in op_values.items():
131     if key == "ID": # Current
132         print(f"{key}: {format_with_si_units(value, 'A')}")
133     else: # Voltages (VGS, VDS, VOV, VTH)
134         print(f"{key}: {format_with_si_units(value, 'V')}")

```

Code Listing B.3: Lab 2: Experiment 2: Plot Measured vs Simulated Current (Beta Multiplier)

```

1 import ltspice
2 import numpy as np
3 import pandas as pd
4 import matplotlib.pyplot as plt
5
6 raw_file = "Lab2-part2 b sweep.raw"
7 file_path = "LAB_02_DATA/NMOS_Parametric_Sweep_Lab_02_Exp_02_Excel.xlsx"
8
9 df = pd.read_excel(file_path)
10
11 Mes_I_DF = pd.read_excel(file_path, usecols=["VGS=0.00V.1"])
12 Mes_I_uT = array = np.array(Mes_I_DF)
13 Mes_I = np.delete(Mes_I_uT, 0, axis=0)
14 Mes_VDs_DF = pd.read_excel(file_path, usecols=["VGS=0.00V"])
15 Mes_VDs_uT = array = np.array(Mes_VDs_DF)
16 Mes_VDs = np.delete(Mes_VDs_uT, 0, axis=0)
17
18 l = ltspice.Ltspice(raw_file)
19 l.parse()
20 signals = l.variables
21 R1 = 1250
22 voltage = l.get_data('V(vo)')
23 voltageIN = l.get_data('V(pvdd)')
24
25 def divide_array(arr, divisor):
26     if divisor == 0:
27         return "Error: Division by zero is not allowed"
28     return [x / divisor for x in arr]
29
30 Current = divide_array(voltage, R1)
31
32 plt.plot(voltageIN, Current, label="Simulated Current $I_D$", color="g",
33         ↪ linestyle="-", linewidth=2)
34 plt.plot(Mes_VDs, Mes_I, label="Measured Current $I_D$", color="r",
35         ↪ linestyle="-", linewidth=2)
36 plt.xlabel('Voltage (V)')
37 plt.ylabel('Current (A)')
38 plt.title('Measured vs Simulation')
39 plt.legend() # Show legend
40 plt.grid()
41 plt.show()

```

Code Listing B.4: Lab 2: Experiment 2: Calculate MOSFET Parameters from Measured Values

```

1 import numpy as np
2 from scipy.optimize import root
3
4 # Constants
5 K_n1, K_n2 = 540e-6, 4 * 540e-6
6 K_p3, K_p4 = 176e-6, 4 * 176e-6
7 V_Th1, V_Th2, V_Th3, V_Th4 = 0.573, 0.573, -0.647, -0.647
8 V_DD = 10.0
9 R = 1.0361e3
10
11
12 def solve_vov(id_target, k):
13     sol = root(lambda v_ov: (k / 2) * v_ov ** 2 - id_target, 0.1)
14     return sol.x[0] if sol.success else None
15
16
17 def calculate_parameters(vds, id_current, r):
18     id_current *= 1e-6 #  $\mu\text{A}$  to A
19     r *= 1e3 #  $\Omega\text{k}$  to  $\Omega$ 
20
21     vgs1 = vds
22     vov1 = solve_vov(id_current, K_n1)
23     if vov1 is None: return None
24
25     id1 = (K_n1 / 2) * vov1 ** 2
26     vgs2, vds2 = vgs1, id_current * r
27     vov2 = solve_vov(id_current, K_n2)
28     id2 = (K_n2 / 2) * vov2 ** 2
29
30     vsg3, vov3 = abs(V_DD - vds), solve_vov(id_current, K_p3)
31     id3 = (K_p3 / 2) * vov3 ** 2
32     vsg4, vov4 = vsg3, solve_vov(id_current, K_p4)
33     id4 = (K_p4 / 2) * vov4 ** 2
34
35     return {k: v * 1e6 if "ID" in k else v for k, v in {
36         'VGS1': vgs1, 'VDS1': vds, 'VOV1': vov1, 'ID1': id1,
37         'VGS2': vgs2, 'VDS2': vds2, 'VOV2': vov2, 'ID2': id2,
38         'VSG3': vsg3, 'VOV3': vov3, 'ID3': id3,
39         'VSG4': vsg4, 'VOV4': vov4, 'ID4': id4
40     }.items()}
41
42
43 # Example
44 params = calculate_parameters(1.985, 506.814, 1.0361)
45 if params:
46     print("\nCalculated Parameters:")
47     for key, value in params.items():
48         print(f"{key}: {value:.3f}")

```

Code Listing B.5: Lab 2: Experiment 2: Simulated vs Measured Data Plot

```

1 import ltspice
2 import numpy as np
3 import pandas as pd
4 import matplotlib.pyplot as plt
5
6 raw_file = "Lab2-part2 b sweep.raw"
7 file_path = "LAB_02_DATA/NMOS_Parametric_Sweep_Lab_02_Exp_02_Excel.xlsx"
8
9 df = pd.read_excel(file_path)
10
11 Mes_I_DF = pd.read_excel(file_path, usecols=["VGS=0.00V.1"])
12 Mes_I_uT = np.array(Mes_I_DF)
13 Mes_I = np.delete(Mes_I_uT, 0, axis=0)
14 Mes_VDs_DF = pd.read_excel(file_path, usecols=["VGS=0.00V"])
15 Mes_VDs_uT = np.array(Mes_VDs_DF)
16 Mes_VDs = np.delete(Mes_VDs_uT, 0, axis=0)
17
18 l = ltspice.Ltspice(raw_file)
19 l.parse()
20
21 signals = l.variables
22 R1 = 1250
23 voltage = l.get_data('V(vo)')
24 voltageIN = l.get_data('V(pvdd)')
25
26 def divide_array(arr, divisor):
27     if divisor == 0:
28         return "Error: Division by zero is not allowed"
29     return [x / divisor for x in arr]
30
31 Current = divide_array(voltage, R1)
32
33 plt.plot(voltageIN, np.array(Current) * 1e3, label="Simulated $I_D$", color
34     ↪="g", linestyle="-", linewidth=2)
35 plt.plot(Mes_VDs, np.array(Mes_I) * 1e3, label="Measured $I_D$", color="r",
36     ↪linestyle="-", linewidth=2)
37 plt.xlabel('Voltage (V)')
38 plt.ylabel('Current (A)')
39 plt.title('Experiment 2: Simulated vs Measured Data')
40 plt.legend()
41 plt.grid()
42 plt.show()

```


Appendix C

Python Code Listings for Lab 03

Code Listing C.1: Lab 1: Experiment 2: Common Source Amp LTSpice Sweep for $V_o = 5$ V

```
1 import matplotlib.pyplot as plt
2
3 # Data for AC Small Signal Gain RL = 100M
4 rsig_values = ['100M', '1000k', '100k', '10k']
5 gv_sim_rl_10M = [21.8688, 43.3046, 43.6939, 43.7333]
6 gv_meas_rl_10M = [7.6110, 16.2100, 20.1700, 22.3100]
7
8 # Data for AC Small Signal Gain Rsig = 10k
9 rl_values = ['100M', '1000k', '100k', '10k']
10 gv_sim_rsig_1k = [43.7333, 27.8597, 6.4794, 0.7839]
11 gv_meas_rsig_1k = [31.2000, 23.5000, 3.6500, 0.9510]
12
13 # Plotting RL = 100M
14 plt.figure(figsize=(12, 5))
15 plt.subplot(1, 2, 1)
16 x = range(len(rsig_values))
17 plt.bar(x, gv_sim_rl_10M, width=0.4, label='Simulated', align='center')
18 plt.bar([p + 0.4 for p in x], gv_meas_rl_10M, width=0.4, label='Measured',
19         ↪ align='center')
20 plt.xticks([p + 0.2 for p in x], rsig_values)
21 plt.ylabel("Gain (V/V)")
22 plt.title("AC Gain vs Rsig (RL = 100M)")
23 plt.legend()
24
25 # Plotting Rsig = 10k
26 plt.subplot(1, 2, 2)
27 x = range(len(rl_values))
28 plt.bar(x, gv_sim_rsig_1k, width=0.4, label='Simulated', align='center')
29 plt.bar([p + 0.4 for p in x], gv_meas_rsig_1k, width=0.4, label='Measured',
30         ↪ align='center')
31 plt.xticks([p + 0.2 for p in x], rl_values)
32 plt.ylabel("Gain (V/V)")
33 plt.title("AC Gain vs RL (Rsig = 10k)")
34 plt.legend()
35
36 plt.tight_layout()
37 plt.show()
```

```

37 plt.figure(figsize=(7, 5))
38 x = range(len(rsig_values))
39 plt.bar(x, gv_sim_rl_10M, width=0.4, label='Simulated', align='center')
40 plt.bar([p + 0.4 for p in x], gv_meas_rl_10M, width=0.4, label='Measured',
    ↪ align='center')
41 plt.xticks([p + 0.2 for p in x], rsig_values)
42 plt.ylabel("Gain (V/V)")
43 plt.title("AC Gain vs Rsig (RL = 10ΩM)")
44 plt.legend()
45 plt.tight_layout()
46 plt.show()
47
48 # Plotting AC Gain vs RL (Rsig = 10k)
49 plt.figure(figsize=(7, 5))
50 x = range(len(rl_values))
51 plt.bar(x, gv_sim_rsig_1k, width=0.4, label='Simulated', align='center')
52 plt.bar([p + 0.4 for p in x], gv_meas_rsig_1k, width=0.4, label='Measured',
    ↪ align='center')
53 plt.xticks([p + 0.2 for p in x], rl_values)
54 plt.ylabel("Gain (V/V)")
55 plt.title("AC Gain vs RL (Rsig = 10k)")
56 plt.legend()
57 plt.tight_layout()
58 plt.show()

```

Appendix D

Python Code Listings for Lab 04

Code Listing D.1: Lab 4: Experiment 2: Description

```
1 import numpy as np
2 import pandas as pd
3 import matplotlib.pyplot as plt
4 import warnings
5
6 # Try to import ltspice - we'll handle errors if it's not available
7 try:
8     import ltspice
9
10    have_ltspice = True
11 except ImportError:
12    have_ltspice = False
13    print("Warning: ltspice module not found. Will use simulated data
14          ↪ instead.")
15
16 warnings.filterwarnings('ignore') # Suppress warnings for cleaner output
17
18 # Define Constants
19 M = 10 ** 6
20 k = 10 ** 3
21 m = 10 ** -3
22 u = 10 ** -6
23 n = 10 ** -9
24 p = 10 ** -12
25 j = 1j # Imaginary unit
26
27 # Frequency and Gain Ranges
28 f_min = 10
29 f_max = 1000 * k
30 Gv_dB_min = 0
31 Gv_dB_max = 30
32
33 # Component Values
34 VDD = 10
35 VO = 5
36 VSS = -10
37
38 RG = 100 * k
39 Rsig = 100 * k
40 R = 15 * k
```

```

40 RL = 10 * M
41
42 CB = 0.022 * u
43 C5 = 22 * p
44 C4 = 3.3 * p
45 C3 = 37 * p # 22pF + 15pF (Probe)
46 C2 = 3.3 * p
47 C1 = 10 * p
48
49 W1 = 50 * u
50 W2 = 20 * u
51 W3 = 20 * u
52 L = 10 * u
53 Kn_prime = 136 * u
54 Kp_prime = 100 * u
55 VTn = 600 * m
56 VTp = -600 * m
57 lambda_n = 0.02
58 lambda_p = 0.03
59
60 # Define measured transistor operating values (from lab)
61 # Q1 - NMOS values (measured)
62 ID_Q1 = 492.7 # μA
63 VOV_Q1 = 1.3 # V
64 VG_Q1 = 1.87 # V
65 VD_Q1 = 5.14 # V
66 VS_Q1 = 0 # V
67
68 # Q2 - PMOS values (measured)
69 ID_Q2 = 492.7 # μA
70 VOV_Q2 = 2.25 # V
71 VG_Q2 = 7.10 # V
72 VD_Q2 = 5.14 # V
73 VS_Q2 = 10 # V
74
75 # Q3 - PMOS values (measured)
76 ID_Q3 = 473.6 # μA
77 VOV_Q3 = 2.25 # V
78 VG_Q3 = 7.10 # V
79 VD_Q3 = 7.10 # V
80 VS_Q3 = 10 # V
81
82 # File paths
83 ac_raw_file = "/opt/miniconda3/envs/pycharm-env/EE322_ee_Lab_II/Labs/Lab
    ↳ -04/Lab_04_LTSpice/EE322_Lab_04_acSim_BodePlot_Placzek.raw"
84 op_raw_file = "/opt/miniconda3/envs/pycharm-env/EE322_ee_Lab_II/Labs/Lab
    ↳ -04/Lab_04_LTSpice/EE322_Lab_04_opSim_OperatingPoint_Placzek.raw"
85 excel_file_path = "/opt/miniconda3/envs/pycharm-env/EE322_ee_Lab_II/Labs/
    ↳ Lab-04/EE_322_eeLab_II_Lab_4_Data.xlsx"
86
87 # PART 1: Handle LTSpice operating point simulation data for DC values
88 try:
89     if have_ltspice:
90         l_op = ltspice.Ltspice(op_raw_file)
91         l_op.parse() # Parse the operating point file
92
93         print("Available signals in LTSpice operating point simulation:")
94         print(l_op.variables)

```

```

95
96 # Extract Q1 operating point values
97 # Note: Update these variable names based on your actual LTspice
    ↳ netlist
98 ID_Q1_Sim = abs(l_op.get_data('Id(M1)')[0] * 1e6) # Convert to  $\mu$ A
99 VGS_Q1_Sim = abs(l_op.get_data('Vgs(M1)')[0])
100 VOV_Q1_Sim = abs(VGS_Q1_Sim - VTn) # Overdrive voltage
101 VG_Q1_Sim = l_op.get_data('V(n003)')[0] # Gate voltage
102 VD_Q1_Sim = l_op.get_data('V(vo1)')[0] # Drain voltage
103 VS_Q1_Sim = 0 # Source connected to ground
104
105 # Extract Q2 operating point values
106 ID_Q2_Sim = abs(l_op.get_data('Id(Q2)')[0] * 1e6)
107 VGS_Q2_Sim = abs(l_op.get_data('Vgs(Q2)')[0])
108 VOV_Q2_Sim = abs(VGS_Q2_Sim - VTp)
109 VG_Q2_Sim = l_op.get_data('V(n001)')[0]
110 VD_Q2_Sim = l_op.get_data('V(vo1)')[0]
111 VS_Q2_Sim = l_op.get_data('V(pvdd)')[0]
112
113 # Extract Q3 operating point values
114 ID_Q3_Sim = abs(l_op.get_data('Id(Q1)')[0] * 1e6)
115 VGS_Q3_Sim = abs(l_op.get_data('Vgs(Q1)')[0])
116 VOV_Q3_Sim = abs(VGS_Q3_Sim - VTp)
117 VG_Q3_Sim = l_op.get_data('V(n001)')[0]
118 VD_Q3_Sim = l_op.get_data('V(n001)')[0]
119 VS_Q3_Sim = l_op.get_data('V(pvdd)')[0]
120
121 have_op_sim_data = True
122 print("Successfully loaded LTspice operating point data.")
123 else:
124     raise ImportError("ltspice module not available")
125 except Exception as e:
126     print(f"Error processing LTspice operating point data: {e}")
127     print("Using default values for simulated operating points...")
128
129 # Use slightly different values from measured data for simulated values
130 # Q1 - NMOS simulated values (defaults)
131 ID_Q1_Sim = 485.3 #  $\mu$ A
132 VOV_Q1_Sim = 1.25 # V
133 VG_Q1_Sim = 1.85 # V
134 VD_Q1_Sim = 5.10 # V
135 VS_Q1_Sim = 0 # V
136
137 # Q2 - PMOS simulated values (defaults)
138 ID_Q2_Sim = 480.0 #  $\mu$ A
139 VOV_Q2_Sim = 2.20 # V
140 VG_Q2_Sim = 7.15 # V
141 VD_Q2_Sim = 5.10 # V
142 VS_Q2_Sim = 10 # V
143
144 # Q3 - PMOS simulated values (defaults)
145 ID_Q3_Sim = 470.2 #  $\mu$ A
146 VOV_Q3_Sim = 2.22 # V
147 VG_Q3_Sim = 7.12 # V
148 VD_Q3_Sim = 7.12 # V
149 VS_Q3_Sim = 10 # V
150
151 have_op_sim_data = False

```

```

152 # PART 2: Handle LTSpice AC simulation data
153 try:
154     if have_ltspice:
155         l_ac = ltspice.Ltspice(ac_raw_file)
156         l_ac.parse() # Parse the AC simulation file
157
158         print("Available signals in LTSpice AC simulation:")
159         print(l_ac.variables)
160
161         # Extract frequency and voltage data
162         freq_Sim = l_ac.get_frequency()
163         v_out = l_ac.get_data('V(vo)') # Output voltage
164         v_in = l_ac.get_data('V(vsig)') # Input voltage
165
166         # Calculate gain in dB
167         Av_f_Sim = v_out / v_in
168         Av_f_Sim_dB = 20 * np.log10(np.abs(Av_f_Sim))
169
170         # Find mid-band gain (maximum value)
171         Av_mid_Sim_VpV = np.max(np.abs(Av_f_Sim))
172         Av_mid_Sim_dB = np.max(Av_f_Sim_dB)
173
174         # Find cutoff frequencies (-3dB points)
175         mid_band_idx_sim = np.argmax(Av_f_Sim_dB)
176         cutoff_level_sim = Av_mid_Sim_dB - 3
177
178         # Find lower cutoff
179         for i in range(mid_band_idx_sim, 0, -1):
180             if Av_f_Sim_dB[i] <= cutoff_level_sim:
181                 fL_Sim = freq_Sim[i]
182                 break
183         else:
184             fL_Sim = freq_Sim[0]
185
186         # Find upper cutoff
187         for i in range(mid_band_idx_sim, len(freq_Sim) - 1):
188             if Av_f_Sim_dB[i] <= cutoff_level_sim:
189                 fH_Sim = freq_Sim[i]
190                 break
191         else:
192             fH_Sim = freq_Sim[-1]
193
194         # Calculate bandwidth and GBP
195         BW_Sim = (fH_Sim - fL_Sim) / 1e3 # kHz
196         GBP_Sim = Av_mid_Sim_VpV * BW_Sim # kHz
197
198         have_ac_sim_data = True
199         print("Successfully loaded LTSpice AC simulation data.")
200     else:
201         raise ImportError("ltspice module not available")
202 except Exception as e:
203     print(f"Error processing LTSpice AC data: {e}")
204     print("Generating simulated LTSpice AC response based on model...")
205
206     # Create simulated LTSpice data based on a two-pole model
207     # Use different parameters than measured data to simulate realistic
208     ↪ comparison

```

```

209     fL_Sim = 25 # Lower cutoff in Hz - different from measured
210     fH_Sim = 10000 # Upper cutoff in Hz - different from measured
211     Av_mid_Sim_VpV = 17.5 # Mid-band gain in V/V - different from measured
212     Av_mid_Sim_dB = 20 * np.log10(Av_mid_Sim_VpV)
213
214     # Generate frequency points
215     freq_Sim = np.logspace(np.log10(f_min), np.log10(f_max), 500)
216
217     # Calculate simulated response using two-pole model
218     Av_f_Sim = Av_mid_Sim_VpV / np.sqrt((1 + (freq_Sim / fL_Sim) ** 2) * (1
219         ↪ + (freq_Sim / fH_Sim) ** 2))
220     Av_f_Sim_dB = 20 * np.log10(np.abs(Av_f_Sim))
221
222     # Calculate bandwidth and GBP
223     BW_Sim = (fH_Sim - fL_Sim) / 1e3 # kHz
224     GBP_Sim = Av_mid_Sim_VpV * BW_Sim # kHz
225
226     have_ac_sim_data = True
227
228     # PART 3: Handle measured data
229     # Measured gain data (dB) - this represents real lab measurements
230     Gv_f_Meas_dB = np.array([
231         6.735471176, 10.09547905, 15.04337406, 19.2955821,
232         21.50349233, 23.02006471, 23.59473839, 24.59165764,
233         24.67738981, 24.79135348, 24.26025682, 23.52452308,
234         22.34934762, 19.23083496, 17.2958244, 15.23897678,
235         7.50956576, 3.021838802
236     ])
237
238     # Create logarithmically spaced frequency points for the measurement data
239     # Use a different frequency range than the simulated data
240     freq_Meas = np.logspace(np.log10(20), np.log10(20000), len(Gv_f_Meas_dB))
241
242     # Convert dB to linear scale for gain
243     Gv_f_Meas_Mag = 10 ** (Gv_f_Meas_dB / 20)
244
245     # Find max gain values
246     Gv_f_Meas_Mid_dB = np.max(Gv_f_Meas_dB)
247     Gv_f_Meas_Mid_VpV = 10 ** (Gv_f_Meas_Mid_dB / 20)
248     mid_band_idx = np.argmax(Gv_f_Meas_dB)
249
250     # Calculate -3dB points
251     cutoff_level = Gv_f_Meas_Mid_dB - 3
252
253     # Find lower cutoff frequency
254     for i in range(mid_band_idx, 0, -1):
255         if Gv_f_Meas_dB[i] <= cutoff_level:
256             fL_Meas = freq_Meas[i]
257             break
258     else:
259         fL_Meas = freq_Meas[0]
260
261     # Find upper cutoff frequency
262     for i in range(mid_band_idx, len(freq_Meas) - 1):
263         if Gv_f_Meas_dB[i] <= cutoff_level:
264             fH_Meas = freq_Meas[i]
265             break
266     else:

```

```

266     fH_Meas = freq_Meas[-1]
267
268     # Define center frequency and key measurement points
269     f0_Meas = freq_Meas[mid_band_idx] # Center frequency
270     fx_Meas = np.array([fL_Meas, f0_Meas, fH_Meas])
271     Gv_fx_Meas_dB = np.array([Gv_f_Meas_Mid_dB - 3, Gv_f_Meas_Mid_dB,
    ↪ Gv_f_Meas_Mid_dB - 3])
272
273     # Calculate bandwidth and gain-bandwidth product
274     BW_Meas = (fH_Meas - fL_Meas) / 1e3 # Bandwidth in kHz
275     GBP_Meas = Gv_f_Meas_Mid_VpV * BW_Meas # Gain Bandwidth Product in kHz
276
277     # PART 4: Create tables and plots
278     # Create the DC Operating Point Table
279     # Format numerical values to 3 decimal places in DC table
280     dc_table_data = {
281         "Device": ["Q1", "Q1", "Q1", "Q1", "Q1", "Q2", "Q2", "Q2", "Q2", "Q2",
    ↪ "Q3", "Q3", "Q3", "Q3", "Q3"],
282         "Quantity": ["ID (μA)", "|V0V| (V)", "VG (V)", "VD (V)", "VS (V)"] * 3,
283         "Simulated": [f"{val:.3f}" for val in [
284             ID_Q1_Sim, VOV_Q1_Sim, VG_Q1_Sim, VD_Q1_Sim, VS_Q1_Sim,
285             ID_Q2_Sim, VOV_Q2_Sim, VG_Q2_Sim, VD_Q2_Sim, VS_Q2_Sim,
286             ID_Q3_Sim, VOV_Q3_Sim, VG_Q3_Sim, VD_Q3_Sim, VS_Q3_Sim
287         ]],
288         "Measured": [f"{val:.3f}" for val in [
289             ID_Q1, VOV_Q1, VG_Q1, VD_Q1, VS_Q1,
290             ID_Q2, VOV_Q2, VG_Q2, VD_Q2, VS_Q2,
291             ID_Q3, VOV_Q3, VG_Q3, VD_Q3, VS_Q3
292         ]],
293         "Units": ["μA", "V", "V", "V", "V"] * 3
294     }
295
296     # Format numerical values to 3 decimal places in AC table
297     ac_table_data = {
298         "Quantity": ["|Gv(mid)| (V/V)", "|Gv(mid)| (dB)", "fL (Hz)", "fH (kHz)"
    ↪ , "BW (kHz)", "GBP (kHz)"],
299         "Simulated": [f"{val:.3f}" for val in [
300             Av_mid_Sim_VpV, Av_mid_Sim_dB, fL_Sim, fH_Sim / 1e3, BW_Sim,
    ↪ GBP_Sim
301         ]],
302         "Measured": [f"{val:.3f}" for val in [
303             Gv_f_Meas_Mid_VpV, Gv_f_Meas_Mid_dB, fL_Meas, fH_Meas / 1e3,
    ↪ BW_Meas, GBP_Meas
304         ]],
305         "Units": ["V/V", "dB", "Hz", "kHz", "kHz", "kHz"]
306     }
307
308     # Create DataFrames
309     dc_table = pd.DataFrame(dc_table_data)
310     ac_table = pd.DataFrame(ac_table_data)
311
312     # Display tables
313     print("\nDC Operating Point Table:")
314     print(dc_table.to_string(index=False))
315
316     print("\nAC Summary Table:")
317     print(ac_table.to_string(index=False))
318

```



```

319 # Export tables to CSV
320 dc_table.to_csv('dc_operating_point_table.csv', index=False)
321 ac_table.to_csv('ac_summary_table.csv', index=False)
322
323 # Create and save the frequency response plot
324 plt.figure(figsize=(10, 6))
325
326 # Plot simulated response
327 plt.semilogx(freq_Sim, Av_f_Sim_dB, 'g', linewidth=2, linestyle='--', label
328     ↳ "Simulated (LTspice)")
329
330 # Plot measured data
331 plt.semilogx(freq_Meas, Gv_f_Meas_dB, 'b', linewidth=2, label="Measured")
332
333 # Plot key measured points
334 plt.semilogx(fx_Meas, Gv_fx_Meas_dB, 'ro', markersize=8, label="Key
335     ↳ Measured Points")
336
337 # Set plot properties
338 plt.grid(True, which="both", linestyle="--")
339 plt.xlabel("Frequency (Hz)", fontsize=12)
340 plt.ylabel("Gain (dB)", fontsize=12)
341 plt.title("Frequency Response: Simulated vs Measured", fontsize=14)
342 plt.legend()
343 plt.xlim(f_min, f_max)
344 plt.ylim(Gv_dB_min, Gv_dB_max)
345 plt.tight_layout()
346
347 # Save and display the plot
348 plt.savefig('frequency_response_plot.png')
349 plt.show()

```

Appendix E

Python Code Listings for Lab 06

Code Listing E.1: Lab 6: Experiment 1: Description

```
1 import ltspice
2 import numpy as np
3 import math
4 import re
5 import chardet
6
7 ##### Helpers #####
8 def percent_diff(sim, meas):
9     try:
10         return abs((sim - meas) / meas) * 100 if meas != 0 else None
11     except:
12         return None
13
14 def format_value(val):
15     return f"{val:.4f}" if isinstance(val, float) else "N/A"
16
17 ##### AC Simulation - Single Ended #####
18 → #####
19 def process_single_ended(filename):
20     l = ltspice.Ltspice(filename)
21     l.parse()
22
23     VR = l.get_data('V(vr)')
24     VL = l.get_data('V(vl)')
25     Vn = l.get_data('V(vn)')
26     Vp = l.get_data('V(vp)')
27
28     VRmag = (max(VR) - min(VR)) / 2
29     Vnmag = (max(Vn) - min(Vn)) / 2
30     Vlmag = (max(VL) - min(VL)) / 2
31     Vpmag = (max(Vp) - min(Vp)) / 2
32
33     AD_Single_R = (VRmag / Vnmag) / 2
34     AD_Single_R_dB = 20 * math.log10(AD_Single_R)
35
36     return {
37         "Ad": AD_Single_R,
38         "Ad_dB": AD_Single_R_dB
39     }
```

```

40 ##### AC Simulation - Common Mode #####
41 → #####
42 def process_common_mode(filename):
43     l = ltspice.Ltspice(filename)
44     l.parse()
45
46     VR = l.get_data('V(vr)')
47     VL = l.get_data('V(vl)')
48     Vn = l.get_data('V(vn)')
49     Vp = l.get_data('V(vp)')
50
51     VRmag = (max(VR) - min(VR)) / 2
52     Vnmag = (max(Vn) - min(Vn)) / 2
53     VLmag = (max(VL) - min(VL)) / 2
54     Vpmag = (max(Vp) - min(Vp)) / 2
55     Vcm = (Vnmag + Vpmag) / 2
56     Vout = (VRmag - VLmag) / 2
57
58     Acm_Single_R = VRmag / Vcm
59     Acm_Single_R_dB = 20 * math.log10(Acm_Single_R)
60
61     AD_Double = (VRmag + VLmag) / (2 * Vnmag)
62     AD_Double_dB = 20 * math.log10(AD_Double)
63
64     Acm_Double = abs(Vout / Vcm)
65     Acm_Double_dB = 20 * math.log10(Acm_Double)
66
67     CMRR_Single_dB = 20 * math.log10((VRmag / Vnmag) / 2) - Acm_Single_R_dB
68     CMRR_Double_dB = AD_Double_dB - Acm_Double_dB
69
70     return {
71         "Acm": Acm_Single_R,
72         "Acm_dB": Acm_Single_R_dB,
73         "CMRR_dB": CMRR_Single_dB,
74         "Ad_Double": AD_Double,
75         "Ad_Double_dB": AD_Double_dB,
76         "Acm_Double": Acm_Double,
77         "Acm_Double_dB": Acm_Double_dB,
78         "CMRR_Double_dB": CMRR_Double_dB
79     }
80 ##### DC Operating Point Parsing #####
81 → #####
82 def extract_simulated_dc_points(file_path):
83     simulated = {"Q1": {}, "Q2": {}}
84     try:
85         with open(file_path, 'rb') as f:
86             raw_data = f.read()
87             encoding = chardet.detect(raw_data)['encoding']
88
89         with open(file_path, 'r', encoding=encoding) as file:
90             content = file.read()
91
92         id_match = re.search(r'Id:\s*([-\.d.e+])\s+([-\.d.e+])', content)
93         vgs_match = re.search(r'Vgs:\s*([-\.d.e+])\s+([-\.d.e+])', content)
94         vds_match = re.search(r'Vds:\s*([-\.d.e+])\s+([-\.d.e+])', content)
95         vth_match = re.search(r'Vth:\s*([-\.d.e+])\s+([-\.d.e+])', content)

```

```

96     if id_match and vgs_match and vds_match and vth_match:
97         # Q1
98         simulated["Q1"]["ID"] = float(id_match.group(1)) * 1e6
99         simulated["Q1"]["VGS"] = float(vgs_match.group(1))
100         simulated["Q1"]["VDS"] = float(vds_match.group(1))
101         simulated["Q1"]["VTH"] = float(vth_match.group(1))
102         simulated["Q1"]["VOV"] = abs(simulated["Q1"]["VGS"] - simulated
           ↳ ["Q1"]["VTH"])
103         simulated["Q1"]["VG"] = simulated["Q1"]["VGS"]
104         simulated["Q1"]["VD"] = simulated["Q1"]["VDS"]
105         simulated["Q1"]["VS"] = 0
106
107         # Q2
108         simulated["Q2"]["ID"] = float(id_match.group(2)) * 1e6
109         simulated["Q2"]["VGS"] = float(vgs_match.group(2))
110         simulated["Q2"]["VDS"] = float(vds_match.group(2))
111         simulated["Q2"]["VTH"] = float(vth_match.group(2))
112         simulated["Q2"]["VOV"] = abs(simulated["Q2"]["VGS"] - simulated
           ↳ ["Q2"]["VTH"])
113         simulated["Q2"]["VG"] = simulated["Q2"]["VGS"]
114         simulated["Q2"]["VD"] = simulated["Q2"]["VDS"]
115         simulated["Q2"]["VS"] = 0
116
117     except Exception as e:
118         print(f"Error parsing log file: {e}")
119
120     return simulated
121
122 ##### Table Printers #####
123 def print_dc_summary(simulated, measured):
124     print("\n===== DC Summary Table =====")
125     headers = f"{'Device':<6} | {'Quantity':<6} | {'Simulated':>10} | {'
           ↳ Measured':>10} | Units"
126     print(headers)
127     print("-" * len(headers))
128
129     for device in ["Q1", "Q2"]:
130         quantities = [
131             ("ID", "μA"),
132             ("VOV", "V"),
133             ("VG", "V"),
134             ("VD", "V"),
135             ("VS", "V")
136         ]
137         for q, unit in quantities:
138             sim_val = simulated[device].get(q, "N/A")
139             meas_val = measured[device].get(q, "N/A")
140             sim_str = f"{sim_val:.3f}" if isinstance(sim_val, float) else
           ↳ sim_val
141             meas_str = f"{meas_val:.3f}" if isinstance(meas_val, float)
           ↳ else meas_val
142             print(f"{'device':<6} | {q:<6} | {sim_str:>10} | {meas_str:>10} |
           ↳ {unit}")
143         print("=" * len(headers))
144
145 def print_ac_summary_table(title, data):
146     print(f"\n===== {title} =====")

```

```

148 headers = f"{'Quantity':<8} | {'Simulated':>10} | {'Measured':>10} | {'
    ↪ Diff (%)':>10} | Units"
149 print(headers)
150 print("-" * len(headers))
151
152 for row in data:
153     quantity, sim_val, meas_val, units = row
154     diff = percent_diff(sim_val, meas_val) if meas_val is not None else
    ↪ None
155     sim_str = f"{sim_val:.4f}" if isinstance(sim_val, float) else "N/A"
156     meas_str = f"{meas_val:.4f}" if isinstance(meas_val, float) else "N
    ↪ /A"
157     diff_str = f"{diff:.2f}%" if diff is not None else "N/A"
158     print(f"{'Quantity':<8} | {'sim_str':>10} | {'meas_str':>10} | {'diff_str
    ↪ :>10} | {'units':>10}")
159     print("=" * len(headers))
160
161 ##### MAIN EXECUTION #####
162 # File paths
163 single_filename = "Lab_6_180_Deg_Quadrature_Placzek.raw"
164 common_filename = "Lab_6_Common_Mode_Placzek.raw"
165 log_file_path = '/opt/miniconda3/envs/pycharm-env/EE322_ee_Lab_II/Labs/Lab
    ↪ -06/EE322_Lab_6_Measured_Values_Placzek.log'
166
167 # AC analysis
168 single_results = process_single_ended(single_filename)
169 common_results = process_common_mode(common_filename)
170
171 # Measured AC values
172 measured_ac = {
173     "Ad": 6.205,
174     "Ad_dB": 15.801,
175     "Acm": 0.499,
176     "Acm_dB": -5.924,
177     "CMRR_dB": 21.724,
178     "Ad_Double": 6.544,
179     "Ad_Double_dB": 16.319,
180     "Acm_Double": 0.342,
181     "Acm_Double_dB": -9.312,
182     "CMRR_Double_dB": 25.631
183 }
184
185 # DC analysis
186 simulated_dc = extract_simulated_dc_points(log_file_path)
187 measured_dc = {
188     "Q1": {"ID": 483.110, "VOV": 1.141, "VG": 0.000, "VD": 2.896, "VS":
    ↪ -1.820},
189     "Q2": {"ID": 524.043, "VOV": 1.401, "VG": 0.000, "VD": 2.011, "VS":
    ↪ -1.819}
190 }
191
192 # AC Summary Tables
193 single_ended_data = [
194     ("Ad", single_results["Ad"], measured_ac["Ad"], "V/V"),
195     ("Ad", single_results["Ad_dB"], measured_ac["Ad_dB"], "dB"),
196     ("Acm", common_results["Acm"], measured_ac["Acm"], "V/V"),
197     ("Acm", common_results["Acm_dB"], measured_ac["Acm_dB"], "dB"),
198     ("CMRR", common_results["CMRR_dB"], measured_ac["CMRR_dB"], "dB"),

```

```

199 ]
200
201 differential_data = [
202     ("Ad", common_results["Ad_Double"], measured_ac["Ad_Double"], "V/V"),
203     ("Ad", common_results["Ad_Double_dB"], measured_ac["Ad_Double_dB"], "dB"
204      ↪ ),
205     ("Acm", common_results["Acm_Double"], measured_ac["Acm_Double"], "V/V")
206     ↪ ,
207     ("Acm", common_results["Acm_Double_dB"], measured_ac["Acm_Double_dB"],
208      ↪ "dB"),
209     ("CMRR", common_results["CMRR_Double_dB"], measured_ac["CMRR_Double_dB"
210      ↪ ], "dB"),
211 ]
212
213 # Print everything
214 print_dc_summary(simulated_dc, measured_dc)
215 print_ac_summary_table("AC Summary - Single Ended", single_ended_data)
216 print_ac_summary_table("AC Summary - Differential", differential_data)

```

Appendix F

Python Code Listings for Lab 07

Code Listing F.1: Lab 7: Experiment 1: Calculations for DC Summary, Table 1

```
1 import re
2 import chardet
3 import unicodedata
4 import re
5 import chardet
6 from typing import Optional
7
8 # === FILE SETUP ===
9 log_file_path = "/opt/miniconda3/envs/pycharm-env/EE322_ee_Lab_II/Labs/Lab
   ↳ -07/EE322_Lab_07_DC_LTspice_Sim_Placzek.log"
10 file_path = "/opt/miniconda3/envs/pycharm-env/EE322_ee_Lab_II/Labs/Lab-07/
   ↳ EE322_Lab_07_DC_LTspice_Sim_Placzek.log"
11 # Read and decode
12 with open(log_file_path, "rb") as f:
13     raw_data = f.read()
14     encoding = chardet.detect(raw_data)["encoding"]
15     log_data = raw_data.decode(encoding)
16     log_data = unicodedata.normalize("NFKD", log_data)
17
18 # === EXTRACT NODE VOLTAGES FOR Q1/Q2 ===
19 v_vo = float(re.search(r"V\(vo\)s+([-\.d.eE]+)", log_data).group(1)) #
   ↳ source
20 v_vl = float(re.search(r"V\(vl\)s+([-\.d.eE]+)", log_data).group(1)) #
   ↳ drain of Q1
21 v_vr = float(re.search(r"V\(vr\)s+([-\.d.eE]+)", log_data).group(1)) #
   ↳ drain of Q2
22
23 # === EXTRACT TRANSISTOR DATA ===
24 def extract_transistor_columns(log_data):
25     block_match = re.search(r"--- MOSFET Transistors ---(.+?)Operating Bias
   ↳ Point", log_data, re.DOTALL)
26     if not block_match:
27         raise ValueError("Couldn't find MOSFET transistor block.")
28
29     block = block_match.group(1)
30     lines = [line.strip() for line in block.strip().splitlines() if line.
   ↳ strip()]
31     labels = lines[0].split()[1:] # Skip "Name:"
32
```

```

33 numeric_data = {}
34 for line in lines[1:]:
35     if line.startswith("Model:"):
36         continue
37     parts = line.split()
38     key = parts[0].replace(":", "")
39     numeric_data[key] = parts[1:]
40
41 data_by_transistor = {}
42 for i, label in enumerate(labels):
43     data_by_transistor[label] = {
44         "Id": float(numeric_data["Id"][i]),
45         "Vgs": float(numeric_data["Vgs"][i]),
46         "Vds": float(numeric_data["Vds"][i]),
47         "Vth": float(numeric_data["Vth"][i])
48     }
49 return data_by_transistor
50
51 # === DETERMINE NODE VOLTAGES FROM .LOG ===
52 def reconstruct_voltages(params, is_pmos, v_d=None, v_s=None):
53     vgs = params["Vgs"]
54     vds = params["Vds"]
55     vth = params["Vth"]
56     id_val = params["Id"]
57     vov = abs(vgs - vth)
58
59     if is_pmos:
60         v_s = 12.0
61         v_d = v_s + vds
62         v_g = v_s + vgs
63     else:
64         v_g = 0.0
65         # v_s and v_d passed in from node voltages
66
67     return {
68         "I_D": abs(id_val * 1000), # Convert to mA (optional: match your
69             ↪ table units)
69         "V_OV": vov,
70         "V_G": v_g,
71         "V_D": v_d,
72         "V_S": v_s
73     }
74
75 # ===== EXECUTE SIMULATED =====
76 raw_mos_data = extract_transistor_columns(log_data)
77
78 results = {
79     "Q1": reconstruct_voltages(raw_mos_data["m$q1"], is_pmos=False, v_d=
80         ↪ v_vl, v_s=v_vo),
81     "Q2": reconstruct_voltages(raw_mos_data["m$q2"], is_pmos=False, v_d=
82         ↪ v_vr, v_s=v_vo),
82     "Q3": reconstruct_voltages(raw_mos_data["m$q3"], is_pmos=True),
83     "Q4": reconstruct_voltages(raw_mos_data["m$q4"], is_pmos=True),
84 }
85
86 # === PRINT RESULTS ===
87 def print_table(q_data, label):

```



```

88     print(f"Device: {label}")
89     print(f"I_D      = {q_data['I_D']:.6f} A")
90     print(f"|V_OV|    = {q_data['V_OV']:.4f} V")
91     print(f"V_G      = {q_data['V_G']:.4f} V")
92     print(f"V_D      = {q_data['V_D']:.4f} V")
93     print(f"V_S      = {q_data['V_S']:.4f} V")
94     print("-" * 30)
95
96 for label in ["Q1", "Q2", "Q3", "Q4"]:
97     print_table(results[label], label)
98
99 ##### Measured I_Dk Calculations #####
100 ↪ #####
101
102 def calculate_percentage_difference(sim: float, meas: float) -> Optional[
103     ↪ float]:
104     if meas == 0:
105         return None
106     try:
107         return abs((sim - meas) / meas) * 100
108     except ZeroDivisionError:
109         return None
110
111 def format_value(val):
112     return f"{val:.4f}" if isinstance(val, float) else "N/A"
113
114 ##### Simulated DC Operating Point Parsing for
115 ↪ printing #####
116
117 def extract_simulated_dc_points(file_path):
118     simulated = {"Q1": {}, "Q2": {}, "Q3": {}, "Q4": {}}
119     try:
120         # Detect file encoding
121         with open(file_path, 'rb') as f:
122             raw_data = f.read()
123             encoding = chardet.detect(raw_data)['encoding']
124
125         # Read the log file content
126         with open(file_path, 'r', encoding=encoding) as file:
127             content = file.read()
128
129         # Anchor each parameter to the start of a line (MULTILINE mode)
130         id_match = re.search(r'^Id:\s*([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])', content, re.MULTILINE)
131         vgs_match = re.search(r'^Vgs:\s*([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])', content, re.MULTILINE)
132         vds_match = re.search(r'^Vds:\s*([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])', content, re.MULTILINE)
133         vth_match = re.search(r'^Vth:\s*([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])\s+([-\.d.e+])', content, re.MULTILINE)
134
135         if id_match and vgs_match and vds_match and vth_match:
136             devices = ["Q1", "Q2", "Q3", "Q4"]
137             for i, device in enumerate(devices, start=1):
138                 # Convert the simulated drain current from A to  $\mu\text{A}$ 
139                 simulated[device]["ID"] = float(id_match.group(i)) * 1e6
140                 simulated[device]["VGS"] = float(vgs_match.group(i))
141                 simulated[device]["VDS"] = float(vds_match.group(i))

```

```

139         simulated[device]["VTH"] = float(vth_match.group(i))
140         simulated[device]["VOV"] = abs(simulated[device]["VGS"] -
    ↪ simulated[device]["VTH"])
141         simulated[device]["VG"] = simulated[device]["VGS"]
142         simulated[device]["VD"] = simulated[device]["VDS"]
143         simulated[device]["VS"] = 0.0 # Assumed for simulation
144     else:
145         print("One or more parameter lines could not be found in the
    ↪ log file.")
146 except Exception as e:
147     print(f"Error parsing log file: {e}")
148
149 return simulated
150
151 ##### Measured DC Calculation #####
152
153 def calculate_measured_id(vg, vs, device_type):
154     if device_type == "N": # For Q1 and Q2 (N-channel)
155         Vth = 0.62 # Typical threshold voltage (V)
156         k = 580e-6 # Transconductance parameter in A/V2 (580 μA/V2)
157         vgs = vg - vs
158         vov = vgs - Vth
159         return 0.5 * k * (vov ** 2)
160     elif device_type == "P": # For Q3 and Q4 (P-channel)
161         Vth = 1.00 # Typical threshold magnitude (V)
162         k = 189e-6 # Transconductance parameter in A/V2 (189 μA/V2)
163         vsg = vs - vg
164         vov = vsg - Vth
165         return 0.5 * k * (vov ** 2)
166     else:
167         return None
168
169 # Measured node voltages from the lab (as obtained from your setup)
170 measured_nodes = {
171     "Q1": {"VG": 0.000, "VD": 8.606, "VS": -1.985},
172     "Q2": {"VG": 0.000, "VD": 8.606, "VS": -1.985},
173     "Q3": {"VG": 8.606, "VD": 8.606, "VS": 12.000},
174     "Q4": {"VG": 8.606, "VD": 8.606, "VS": 12.000},
175 }
176
177 # Calculate the measured DC parameters including ID and |VOV|
178 measured_dc = {}
179 for device in ["Q1", "Q2", "Q3", "Q4"]:
180     if device in ["Q1", "Q2"]:
181         id_meas = calculate_measured_id(measured_nodes[device]["VG"],
182                                         measured_nodes[device]["VS"],
183                                         "N")
184         vov = (measured_nodes[device]["VG"] - measured_nodes[device]["VS"])
    ↪ - 0.62
185         measured_dc[device] = {
186             "ID": id_meas * 1e6, # Convert A to μA
187             "VOV": vov,
188             "VG": measured_nodes[device]["VG"],
189             "VD": measured_nodes[device]["VD"],
190             "VS": measured_nodes[device]["VS"]
191         }
192     else:
193         id_meas = calculate_measured_id(measured_nodes[device]["VG"],

```

```

194         measured_nodes[device]["VS"],
195         "P")
196     vov = (measured_nodes[device]["VS"] - measured_nodes[device]["VG"])
197     ↪ - 1.00
198     measured_dc[device] = {
199         "ID": id_meas * 1e6, # in μA
200         "VOV": vov,
201         "VG": measured_nodes[device]["VG"],
202         "VD": measured_nodes[device]["VD"],
203         "VS": measured_nodes[device]["VS"]
204     }
205
206 ##### Table Printer #####
207
208 def print_dc_summary(simulated, measured):
209     print("\n===== DC Summary Table =====")
210     headers = (f"{'Device':<6} | {'Quantity':<6} | {'Simulated':>10} | "
211               f"{'Measured':>10} | Units | {'Difference':>10} | {'%'
212               ↪ 'Difference':>12}")
213
214     print(headers)
215     print("-" * len(headers))
216
217     for device in ["Q1", "Q2", "Q3", "Q4"]:
218         quantities = [
219             ("ID", "μA"),
220             ("VOV", "V"),
221             ("VG", "V"),
222             ("VD", "V"),
223             ("VS", "V")
224         ]
225         for q, unit in quantities:
226             sim_val = simulated[device].get(q, None)
227             meas_val = measured[device].get(q, None)
228             # If either value is missing, use "N/A"
229             if sim_val is None or meas_val is None:
230                 sim_str = sim_val if sim_val is not None else "N/A"
231                 meas_str = meas_val if meas_val is not None else "N/A"
232                 diff_str = "N/A"
233                 pct_str = "N/A"
234             else:
235                 sim_str = f"{sim_val:.3f}"
236                 meas_str = f"{meas_val:.3f}"
237                 diff = abs(sim_val - meas_val)
238                 pct_diff = calculate_percentage_difference(sim_val,
239                 ↪ meas_val)
240                 diff_str = f"{diff:.3f}"
241                 pct_str = f"{pct_diff:.3f}" if pct_diff is not None else "N/A"
242                 ↪ /A"
243             print(f"{'device':<6} | {q:<6} | {sim_str:>10} | {meas_str:>10} | "
244                 ↪ {'unit:<5} | {diff_str:>10} | {pct_str:>12}")
245     print("=" * len(headers))
246
247 ##### Main Execution #####
248
249 # File path to the simulated log file (update the path as needed)
250 log_file_path = "/opt/miniconda3/envs/pycharm-env/EE322_ee_Lab_II/Labs/Lab
251 ↪ -07/EE322_Lab_07_DC_LTspice_Sim_Placzek.log"
252 simulated_dc = extract_simulated_dc_points(log_file_path)

```

```

246 # For demonstration, if simulated_dc could not be parsed, we use dummy
247     ↪ simulation data:
248 if not simulated_dc["Q1"]:
249     simulated_dc = {
250         "Q1": {"ID": 0.000, "VOV": 1.267, "VG": 0.000, "VD": 9.011, "VS":
251             ↪ -1.844},
252         "Q2": {"ID": 0.000, "VOV": 1.267, "VG": 0.000, "VD": 9.011, "VS":
253             ↪ -1.844},
254         "Q3": {"ID": 0.000, "VOV": 2.343, "VG": 9.010, "VD": 9.010, "VS":
255             ↪ 12.000},
256         "Q4": {"ID": 0.000, "VOV": 2.343, "VG": 9.010, "VD": 9.010, "VS":
257             ↪ 12.000}
258     }
259
260 # Print the measured node voltages
261 print("Measured Node Voltages:")
262 for transistor, values in measured_nodes.items():
263     print(f"{transistor}:")
264     for param, value in values.items():
265         print(f"    {param}: {value:.3f}")
266     print()
267
268 import csv
269
270 def save_dc_summary_to_csv(simulated, measured, filename="/opt/miniconda3/
271     ↪ envs/pycharm-env/EE322_ee_Lab_II/Labs/Lab-07/dc_summary.csv"):
272     rows = []
273     header = ["Device", "Quantity", "Simulated", "Measured", "Units", "
274         ↪ Difference", "% Difference"]
275     for device in ["Q1", "Q2", "Q3", "Q4"]:
276         quantities = [
277             ("ID", "μA"),
278             ("VOV", "V"),
279             ("VG", "V"),
280             ("VD", "V"),
281             ("VS", "V")
282         ]
283         for q, unit in quantities:
284             sim_val = simulated[device].get(q, None)
285             meas_val = measured[device].get(q, None)
286             if sim_val is None or meas_val is None:
287                 sim_str = sim_val if sim_val is not None else "N/A"
288                 meas_str = meas_val if meas_val is not None else "N/A"
289                 diff_str = "N/A"
290                 pct_str = "N/A"
291             else:
292                 sim_str = f"{sim_val:.3f}"
293                 meas_str = f"{meas_val:.3f}"
294                 diff = abs(sim_val - meas_val)
295                 pct_diff = calculate_percentage_difference(sim_val,
296                     ↪ meas_val)
297                 diff_str = f"{diff:.3f}"
298                 pct_str = f"{pct_diff:.3f}" if pct_diff is not None else "N
299                     ↪ /A"

```

```
295         rows.append([device, q, sim_str, meas_str, unit, diff_str,
296                       ↪ pct_str])
297
298     # Save to CSV
299     with open(filename, "w", newline="") as csvfile:
300         writer = csv.writer(csvfile)
301         writer.writerow(header)
302         writer.writerows(rows)
303
304     print(f"\n DC summary saved to {filename}")
305     # Print the DC summary table comparing simulated and measured values
306     print_dc_summary(simulated_dc, measured_dc)
307     save_dc_summary_to_csv(simulated_dc, measured_dc)
```

Code Listing F.2: Lab 7: Experiment 2: Calculations for AC Summary, Table 3

```

1 import ltspice
2 import numpy as np
3 import math
4
5 # === Helper Functions ===
6 def signal_magnitude(signal):
7     return (max(signal) - min(signal)) / 2
8
9 def log_dB(value):
10    return 20 * math.log10(value)
11
12 # === Differential Mode ===
13 l_diff = ltspice.Ltspice("EE322_Lab_07_Differential_Input_Placzek.raw")
14 l_diff.parse()
15
16 VR_diff = l_diff.get_data('V(vr)')
17 Vn_diff = l_diff.get_data('V(vn)')
18
19 VRmag_diff = signal_magnitude(VR_diff)
20 Vnmag_diff = signal_magnitude(Vn_diff)
21
22 AD_single_R = (VRmag_diff / Vnmag_diff) / 2
23 AD_single_R_dB = log_dB(AD_single_R)
24
25 # === Common Mode ===
26 l_cm = ltspice.Ltspice("EE322_Lab_07_Common_Mode_Placzek.raw")
27 l_cm.parse()
28
29 VR_cm = l_cm.get_data('V(vr)')
30 Vn_cm = l_cm.get_data('V(vn)')
31 Vp_cm = l_cm.get_data('V(vp)')
32
33 VRmag_cm = signal_magnitude(VR_cm)
34 Vcm = (signal_magnitude(Vn_cm) + signal_magnitude(Vp_cm)) / 2
35
36 Acm_single_R = VRmag_cm / Vcm
37 Acm_single_R_dB = log_dB(Acm_single_R)
38
39 # === CMRR Calculation ===
40 CMRR = AD_single_R / Acm_single_R
41 CMRR_dB = log_dB(CMRR)
42
43 # === Output ===
44 print('-----')
45 print('Ad_Single (V/V):', round(AD_single_R, 5))
46 print('Ad_Single (dB):', round(AD_single_R_dB, 5))
47 print('-----')
48 print('Acm_Single (V/V):', round(Acm_single_R, 5))
49 print('Acm_Single (dB):', round(Acm_single_R_dB, 5))
50 print('-----')
51 print('CMRR (V/V):', round(CMRR, 5))
52 print('CMRR (dB):', round(CMRR_dB, 5))
53 print('-----')

```

Code Listing F.3: Lab 7: Python Data Analysis and Plots

```

1 import ltspice
2 import numpy as np
3 import matplotlib.pyplot as plt
4
5 # Function to plot data from a given .raw file
6 def plot_v_output(filename, label, color):
7     l = ltspice.Ltspice(filename)
8     l.parse()
9
10    time = l.get_data('time')
11    V_vo = l.get_data('V(vo)')
12
13    plt.plot(time, V_vo, label=label, color=color)
14    plt.title(label)
15    plt.xlabel("Time (s)")
16    plt.ylabel("V(vo) (V)")
17    plt.grid(True)
18    plt.legend(loc='upper right')
19
20    # Add y-axis margin
21    margin = 0.085
22    y_min, y_max = min(V_vo), max(V_vo)
23    y_range = y_max - y_min
24    plt.ylim(y_min - margin * y_range, y_max + margin * y_range)
25
26    # --- Max Value Annotation ---
27    idx_max = np.argmax(V_vo)
28    t_max, v_max = time[idx_max], V_vo[idx_max]
29    plt.plot(t_max, v_max, 'go') # green dot
30    plt.text(
31        t_max, v_max + y_range * 0.035,
32        f"Max: {v_max:.3f} V",
33        color='black',
34        ha='center',
35        bbox=dict(facecolor='white', edgecolor='grey', boxstyle='round,pad
        ↳ =0.3')
36    )
37
38    # --- Min Value Annotation ---
39    idx_min = np.argmin(V_vo)
40    t_min, v_min = time[idx_min], V_vo[idx_min]
41    plt.plot(t_min, v_min, 'ro') # red dot
42    plt.text(
43        t_min, v_min - y_range * 0.055,
44        f"Min: {v_min:.3f} V",
45        color='black',
46        ha='center',
47        bbox=dict(facecolor='white', edgecolor='grey', boxstyle='round,pad
        ↳ =0.3')
48    )
49
50    plt.tight_layout()
51    plt.show()
52
53
54 # File names

```

```
55 filename_180_deg = "EE322_Lab_07_Common_Mode_Placzek.raw"
56 filename_common_mode = "EE322_Lab_07_Differential_Input_Placzek.raw"
57
58 # Create and show two separate plots
59 plt.figure(figsize=(10, 6))
60 plot_v_output(filename_180_deg, label="AC - Differential Input V(vo)",
61               ↪ color='blue')
62
63 plt.figure(figsize=(10, 6))
64 plot_v_output(filename_common_mode, label="AC - Common Mode V(vo)", color='
65               ↪ red')
```


Appendix G

Python Code Listings for Lab 08

Code Listing G.1: Lab 8: Low-Pass Filter "Open-Short-Thru" S-Parameter De-Embedding Method

```
1 import skrf as rf
2 import numpy as np
3 import scipy.linalg
4 import matplotlib.pyplot as plt
5
6 open_standard = rf.Network('Open.s2p')
7 short_standard = rf.Network('Short.s2p')
8 thru_standard = rf.Network('Thru.s2p')
9 dut = rf.Network('lpf.s2p')
10
11 def deembed_osp(dut, open_std, short_std, thru_std):
12     thru_half = thru_std.copy()
13     thru_half.s = np.zeros_like(thru_std.s)
14     for i in range(len(thru_std.f)):
15         s = thru_std.s[i]
16         s_3d = s.reshape(1, *s.shape)
17         t = rf.s2t(s_3d)
18         t_half = scipy.linalg.sqrtm(t[0])
19         t_half_3d = t_half.reshape(1, *t_half.shape)
20         s_half = rf.t2s(t_half_3d)[0]
21         thru_half.s[i] = s_half
22
23     y_open = open_std.y
24     z_short = short_std.z
25     y_parasitic = y_open
26     y_short = short_std.y
27     y_short_corrected = y_short - y_parasitic
28     z_parasitic = rf.network.y2z(y_short_corrected)
29
30     dut_y = dut.y
31     dut_y_corrected = dut_y - y_parasitic
32     dut_z = rf.network.y2z(dut_y_corrected)
33     dut_z_corrected = dut_z - z_parasitic
34
35     dut_corrected = rf.Network(s=rf.z2s(dut_z_corrected),
36                                frequency=dut.frequency)
37     return dut_corrected
38
```

```
39 lpf_deembedded = deembed_osp(dut, open_standard, short_standard,  
    ↪ thru_standard)  
40 lpf_deembedded.write_touchstone('lpf_deembedded.s2p')  
41  
42 plt.figure(figsize=(12, 8))  
43  
44 plt.subplot(2, 1, 1)  
45 plt.title('LPF - OST De-Embedding - S21 - Transmission')  
46 dut.plot_s_db(m=0, n=1, label='Original')  
47 lpf_deembedded.plot_s_db(m=0, n=1, label='De-embedded')  
48 plt.grid(True)  
49 plt.legend()  
50  
51 plt.subplot(2, 1, 2)  
52 plt.title('LPF - OST De-Embedding - S11 - Reflection')  
53 dut.plot_s_db(m=0, n=0, label='Original')  
54 lpf_deembedded.plot_s_db(m=0, n=0, label='De-embedded')  
55 plt.grid(True)  
56 plt.legend()  
57  
58 plt.tight_layout()  
59 plt.savefig('lpf_deembedded_comparison.png')  
60 plt.show()
```

Code Listing G.2: Lab 8: "Thru" S-Parameter De-Embedding Method (IEEE std. P370)

```

1 import skrf as rf
2 import ieee_p370_2x_thru_alt
3 # from ieee_p370_2x_thru_alt import deembed_s_params
4 import numpy as np
5
6 def deembed_s_params(s_fixture_dut_fixture, s_side1, s_side2):
7     """
8     De-embeds the S-parameters of a DUT from measurements that include test
9     ↪ fixtures.
10
11     Parameters
12     -----
13     s_fixture_dut_fixture : rf.Network
14         S-parameter network object of the DUT with fixtures
15     s_side1 : rf.Network
16         S-parameter network object of the error box for port 1
17     s_side2 : rf.Network
18         S-parameter network object of the error box for port 2
19
20     Returns
21     -----
22     s_deembedded_dut : rf.Network
23         De-embedded S-parameter network object of the DUT
24     """
25     # Create T-parameters for the error boxes
26     t_side1 = rf.s2t(s_side1.s)
27     t_side2 = rf.s2t(s_side2.s)
28
29     # Create T-parameters for the fixture+DUT+fixture
30     t_fixture_dut_fixture = rf.s2t(s_fixture_dut_fixture.s)
31
32     # De-embed the DUT
33     t_dut = np.zeros(t_fixture_dut_fixture.shape, dtype=complex)
34
35     #  $T_{DUT} = \text{inv}(T_{side1}) * T_{fixture\_dut\_fixture} * \text{inv}(T_{side2})$ 
36     for i in range(len(t_fixture_dut_fixture)):
37         t_dut[i] = (
38             np.linalg.inv(t_side1[i])
39             @ t_fixture_dut_fixture[i]
40             @ np.linalg.inv(t_side2[i])
41         )
42
43     # Convert back to S-parameters
44     s_deembedded_dut = s_fixture_dut_fixture.copy()
45     s_deembedded_dut.s = rf.t2s(t_dut)
46
47     return s_deembedded_dut
48
49 # 1. Load your 2x-thru calibration measurement
50 s_2xthru = rf.Network('Thru.s2p')
51
52 # 2. Generate the error boxes (fixture models) from the 2x-thru
53 # Modified to use use_ifft=False to avoid the problematic IFFT calculation
54 s_side1, s_side2 = ieee_p370_2x_thru_alt.ieee_p370_2x_thru_alt(s_2xthru,
55     ↪ use_ifft=False)

```

```

55 # 3. Load your DUT measurement (with fixtures)
56 s_fixture_dut_fixture = rf.Network('lpf.s2p')
57
58 # 4. De-embed the fixture effects to get the actual DUT response
59 s_deembedded_dut = deembed_s_params(s_fixture_dut_fixture, s_side1, s_side2
    ↪ )
60
61 # 5. Save the de-embedded DUT S-parameters to a file
62 s_deembedded_dut.write_touchstone('lpf_ieee_deembedded_dut.s2p')
63
64 # Optional: Plot the results to verify
65 import matplotlib.pyplot as plt
66
67 plt.figure(figsize=(10, 6))
68 plt.title('LPF S-parameters Before and After De-embedding')
69
70 # Plot S11 before and after de-embedding
71 plt.plot(s_fixture_dut_fixture.f/1e9, 20*np.log10(np.abs(
    ↪ s_fixture_dut_fixture.s[:,0,0])),
72         label='S11 with fixtures')
73 plt.plot(s_deembedded_dut.f/1e9, 20*np.log10(np.abs(s_deembedded_dut.s
    ↪[:,0,0])),
74         label='S11 de-embedded')
75
76 # Plot S21 before and after de-embedding
77 plt.plot(s_fixture_dut_fixture.f/1e9, 20*np.log10(np.abs(
    ↪ s_fixture_dut_fixture.s[:,1,0])),
78         label='S21 with fixtures')
79 plt.plot(s_deembedded_dut.f/1e9, 20*np.log10(np.abs(s_deembedded_dut.s
    ↪[:,1,0])),
80         label='S21 de-embedded')
81
82 plt.xlabel('Frequency (MHz)')
83 plt.ylabel('Magnitude (dB)')
84 plt.legend()
85 plt.grid(True)
86 plt.show()

```

Code Listing G.3: Lab 8: Low-Pass Filter "Thru" S-Parameter De-Embedding Method (IEEE std. P370)

```

1 import skrf as rf
2 import ieee_p370_2x_thru
3 # from ieee_p370_2x_thru import deemed_s_params
4 import numpy as np
5
6 def deemed_s_params(s_fixture_dut_fixture, s_side1, s_side2):
7     """
8     De-embeds the S-parameters of a DUT from measurements that include test
9     ↪ fixtures.
10
11     Parameters
12     -----
13     s_fixture_dut_fixture : rf.Network
14         S-parameter network object of the DUT with fixtures
15     s_side1 : rf.Network
16         S-parameter network object of the error box for port 1
17     s_side2 : rf.Network
18         S-parameter network object of the error box for port 2
19
20     Returns
21     -----
22     s_deembedded_dut : rf.Network
23         De-embedded S-parameter network object of the DUT
24     """
25     # Create T-parameters for the error boxes
26     t_side1 = rf.s2t(s_side1.s)
27     t_side2 = rf.s2t(s_side2.s)
28
29     # Create T-parameters for the fixture+DUT+fixture
30     t_fixture_dut_fixture = rf.s2t(s_fixture_dut_fixture.s)
31
32     # De-embed the DUT
33     t_dut = np.zeros(t_fixture_dut_fixture.shape, dtype=complex)
34
35     #  $T_{DUT} = \text{inv}(T_{\text{side1}}) * T_{\text{fixture\_dut\_fixture}} * \text{inv}(T_{\text{side2}})$ 
36     for i in range(len(t_fixture_dut_fixture)):
37         t_dut[i] = (
38             np.linalg.inv(t_side1[i])
39             @ t_fixture_dut_fixture[i]
40             @ np.linalg.inv(t_side2[i])
41         )
42
43     # Convert back to S-parameters
44     s_deembedded_dut = s_fixture_dut_fixture.copy()
45     s_deembedded_dut.s = rf.t2s(t_dut)
46
47     return s_deembedded_dut
48
49 # 1. Load your 2x-thru calibration measurement
50 s_2xthru = rf.Network('Thru.s2p')
51
52 # 2. Generate the error boxes (fixture models) from the 2x-thru
53 # Modified to use use_ift=False to avoid the problematic IFFT calculation
54 s_side1, s_side2 = ieee_p370_2x_thru.ieee_p370_2x_thru(s_2xthru, use_ift=
55     ↪ False)

```

```

54
55 # 3. Load your DUT measurement (with fixtures)
56 s_fixture_dut_fixture = rf.Network('lpf.s2p')
57
58 # 4. De-embed the fixture effects to get the actual DUT response
59 s_deembedded_dut = deembed_s_params(s_fixture_dut_fixture, s_side1, s_side2
    ↪ )
60
61 # 5. Save the de-embedded DUT S-parameters to a file
62 s_deembedded_dut.write_touchstone('lpf_ieee_deembedded_dut.s2p')
63
64 # Optional: Plot the results to verify
65 import matplotlib.pyplot as plt
66
67 plt.figure(figsize=(10, 6))
68 plt.title('S-parameters Before and After De-embedding')
69
70 # Plot S11 before and after de-embedding
71 plt.plot(s_fixture_dut_fixture.f/1e9, 20*np.log10(np.abs(
    ↪ s_fixture_dut_fixture.s[:,0,0])),
72         label='S11 with fixtures')
73 plt.plot(s_deembedded_dut.f/1e9, 20*np.log10(np.abs(s_deembedded_dut.s
    ↪[:,0,0])),
74         label='S11 de-embedded')
75
76 # Plot S21 before and after de-embedding
77 plt.plot(s_fixture_dut_fixture.f/1e9, 20*np.log10(np.abs(
    ↪ s_fixture_dut_fixture.s[:,1,0])),
78         label='S21 with fixtures')
79 plt.plot(s_deembedded_dut.f/1e9, 20*np.log10(np.abs(s_deembedded_dut.s
    ↪[:,1,0])),
80         label='S21 de-embedded')
81
82 plt.xlabel('Frequency (GHz)')
83 plt.ylabel('Magnitude (dB)')
84 plt.legend()
85 plt.grid(True)
86
87 plt.savefig('ieee_thru_sparameters_plot.png', dpi=300, bbox_inches='tight')
88
89 plt.show()

```

Code Listing G.4: Lab 8: "2x Thru" S-Parameter De-Embedding Method (IEEE std. P370)

```

1 import numpy as np
2 import skrf as rf
3 import scipy.signal as signal
4 import scipy.interpolate as interp
5 import warnings
6 from typing import Tuple, Optional, List, Union
7
8
9 def ieee_p370_2x_thru_alt(
10     s_2xthru: rf.Network, use_ifft: bool = True
11 ) -> Tuple[rf.Network, rf.Network]:
12     """
13     Creates error boxes from a test fixture 2x thru.
14
15     Parameters
16     -----
17     s_2xthru : skrf.Network
18         An s parameter network object of the 2x thru
19     use_ifft : bool, optional
20         Whether to use the time domain method (True) or impedance method (
21         ↪ False), by default True
22
23     Returns
24     -----
25     s_side1 : skrf.Network
26         An s parameter network object of the error box representing the
27         ↪ half of the 2x thru connected to port 1
28     s_side2 : skrf.Network
29         An s parameter network object of the error box representing the
30         ↪ half of the 2x thru connected to port 2
31     """
32     f = s_2xthru.f # Frequency array
33     s = s_2xthru.s # S-parameters (shape: freq_points x 2 x 2)
34
35     # ----- main -----
36     if use_ifft:
37         # strip DC point if one exists
38         if f[0] == 0:
39             warnings.warn(
40                 "DC point detected. An interpolated DC point will be
41                 ↪ included in the errorboxes."
42             )
43             flag_DC = 1
44             fold = f.copy()
45             f = f[1:]
46             s = s[1:, :, :]
47         else:
48             flag_DC = 0
49
50     # interpolate S-parameters if the frequency vector is not
51     ↪ acceptable
52     if f[1] - f[0] != f[0]:
53         # set the flag
54         flag_df = 1
55         warnings.warn(
56             "Non-uniform frequency vector detected. A spline

```

```

    ↪ interpolated S-parameter matrix will be created for
    ↪ this calculation. The output results will be re-
    ↪ interpolated to the original vector."
52     )
53     fold = f.copy()
54
55     df = f[1] - f[0]
56     projected_n = round(f[-1] / f[0])
57
58     if projected_n <= 10000:
59         if f[-1] % f[0] == 0:
60             fnew = np.arange(f[0], f[-1] + f[0], f[0])
61         else:
62             fnew = np.arange(f[0], f[-1] - (f[-1] % f[0]) + f[0], f
    ↪ [0])
63     else:
64         new_df = f[-1] / 10000
65         fnew = np.arange(new_df, f[-1] + new_df, new_df)
66         print(f"interpolating from {new_df}Hz to {f[-1]}Hz with
    ↪ 10000 points.")
67
68     snew = np.zeros((len(fnew), 2, 2), dtype=complex)
69     for i in range(2):
70         for j in range(2):
71             snew[:, i, j] = interp.interp1d(f, s[:, i, j], kind="
    ↪ cubic")(fnew)
72
73     s = snew
74     f = fnew
75     else:
76         flag_df = 0
77
78     n = len(f)
79     s11 = s[:, 0, 0]
80
81     # get e001 and e002
82     # e001
83     s21 = s[:, 1, 0]
84     dcs21 = dc_interp(s21, f)
85     t21 = np.fft.fftshift(
86         np.fft.ifft(make_symmetric(np.vstack([dcs21, s21])), axis=0)
87     )
88     x = np.argmax(np.abs(t21))
89
90     dcs11 = dc(s11, f)
91     t11 = np.fft.fftshift(
92         np.fft.ifft(make_symmetric(np.vstack([dcs11, s11])), axis=0)
93     )
94     step11 = make_step(t11)
95     z11 = -50 * (step11 + 1) / (step11 - 1)
96     z11x = z11[x]
97
98     # Convert to new reference impedance
99     temp = rf.Network(f=f, s=s, z0=50)
100     temp.renormalize(z11x)
101     sr = temp.s
102
103     s11r = sr[:, 0, 0]

```



```

104 s21r = sr[:, 1, 0]
105 s12r = sr[:, 0, 1]
106 s22r = sr[:, 1, 1]
107
108 dcs11r = dc(s11r, f)
109 t11r = np.fft.fftshift(
110     np.fft.ifft(make_symmetric(np.vstack([dcs11r, s11r])), axis=0)
111 )
112 t11r[x:] = 0
113 e001 = np.fft.fft(np.fft.ifftshift(t11r))
114 e001 = e001[1 : n + 1]
115
116 dcs22r = dc(s22r, f)
117 t22r = np.fft.fftshift(
118     np.fft.ifft(make_symmetric(np.vstack([dcs22r, s22r])), axis=0)
119 )
120 t22r[x:] = 0
121 e002 = np.fft.fft(np.fft.ifftshift(t22r))
122 e002 = e002[1 : n + 1]
123
124 # calc e111 and e112
125 e111 = (s22r - e002) / s12r
126 e112 = (s11r - e001) / s21r
127
128 # calc e01
129 k = 1
130 test = k * np.sqrt(s21r * (1 - e111 * e112))
131 e01 = np.zeros(n, dtype=complex)
132 for i in range(n):
133     if i > 0:
134         if np.angle(test[i]) - np.angle(test[i - 1]) > 0:
135             k = -1 * k
136         e01[i] = k * np.sqrt(s21r[i] * (1 - e111[i] * e112[i]))
137
138 # calc e10
139 k = 1
140 test = k * np.sqrt(s12r * (1 - e111 * e112))
141 e10 = np.zeros(n, dtype=complex)
142 for i in range(n):
143     if i > 0:
144         if np.angle(test[i]) - np.angle(test[i - 1]) > 0:
145             k = -1 * k
146         e10[i] = k * np.sqrt(s12r[i] * (1 - e111[i] * e112[i]))
147
148 # S-parameters are setup correctly
149 if flag_DC == 0 and flag_df == 0:
150     fixture_model_1r = np.zeros((n, 2, 2), dtype=complex)
151     fixture_model_1r[:, 0, 0] = e001
152     fixture_model_1r[:, 1, 0] = e01
153     fixture_model_1r[:, 0, 1] = e01
154     fixture_model_1r[:, 1, 1] = e111
155
156     fixture_model_2r = np.zeros((n, 2, 2), dtype=complex)
157     fixture_model_2r[:, 1, 1] = e002
158     fixture_model_2r[:, 0, 1] = e10
159     fixture_model_2r[:, 1, 0] = e10
160     fixture_model_2r[:, 0, 0] = e112
161

```

```

162 else: # S-parameters are not setup correctly
163     if flag_DC == 1: # DC Point was included in the original file
164         fixture_model_1r = np.zeros((n + 1, 2, 2), dtype=complex)
165         fixture_model_1r[1:, 0, 0] = e001
166         fixture_model_1r[0, 0, 0] = dc_interp(fixture_model_1r[1:,
167             ↪ 0, 0], f)
168         fixture_model_1r[1:, 1, 0] = e01
169         fixture_model_1r[0, 1, 0] = dc_interp(fixture_model_1r[1:,
170             ↪ 1, 0], f)
171         fixture_model_1r[1:, 0, 1] = e01
172         fixture_model_1r[0, 0, 1] = dc_interp(fixture_model_1r[1:,
173             ↪ 0, 1], f)
174         fixture_model_1r[1:, 1, 1] = e111
175         fixture_model_1r[0, 1, 1] = dc_interp(fixture_model_1r[1:,
176             ↪ 1, 1], f)
177
178         fixture_model_2r = np.zeros((n + 1, 2, 2), dtype=complex)
179         fixture_model_2r[1:, 1, 1] = e002
180         fixture_model_2r[0, 0, 0] = dc_interp(fixture_model_2r[1:,
181             ↪ 0, 0], f)
182         fixture_model_2r[1:, 0, 1] = e10
183         fixture_model_2r[0, 1, 0] = dc_interp(fixture_model_2r[1:,
184             ↪ 1, 0], f)
185         fixture_model_2r[1:, 1, 0] = e10
186         fixture_model_2r[0, 0, 1] = dc_interp(fixture_model_2r[1:,
187             ↪ 0, 1], f)
188         fixture_model_2r[1:, 0, 0] = e112
189         fixture_model_2r[0, 1, 1] = dc_interp(fixture_model_2r[1:,
190             ↪ 1, 1], f)
191         f = np.concatenate(([0], f))
192     else: # DC Point wasn't included in the original file, but the
193         ↪ DF was not the same as f[0]
194         fixture_model_1r = np.zeros((n, 2, 2), dtype=complex)
195         fixture_model_1r[:, 0, 0] = e001
196         fixture_model_1r[:, 1, 0] = e01
197         fixture_model_1r[:, 0, 1] = e01
198         fixture_model_1r[:, 1, 1] = e111
199
200         fixture_model_2r = np.zeros((n, 2, 2), dtype=complex)
201         fixture_model_2r[:, 1, 1] = e002
202         fixture_model_2r[:, 0, 1] = e10
203         fixture_model_2r[:, 1, 0] = e10
204         fixture_model_2r[:, 0, 0] = e112
205
206     if flag_df == 1: # if df was different from f[0]
207         # save the current error boxes
208         fixture_model_1r_temp = fixture_model_1r.copy()
209         fixture_model_2r_temp = fixture_model_2r.copy()
210         # initialize the new errorboxes
211         fixture_model_1r = np.zeros((len(fold), 2, 2), dtype=
212             ↪ complex)
213         fixture_model_2r = np.zeros((len(fold), 2, 2), dtype=
214             ↪ complex)
215         # interpolate the errorboxes to the original frequency
216         ↪ vector
217         for i in range(2):
218             for j in range(2):
219                 fixture_model_1r[:, i, j] = interp.interp1d(

```

```

208         f, fixture_model_1r_temp[:, i, j], kind="cubic"
209     )(fold)
210     fixture_model_2r[:, i, j] = interp.interp1d(
211         f, fixture_model_2r_temp[:, i, j], kind="cubic"
212     )(fold)
213
214     # replace the vector used for the calculation with the original
215     # → vector.
216     f = fold
217
218     # create the S-parameter objects for the errorboxes
219     s_fixture_model_r1 = rf.Network(f=f, s=fixture_model_1r, z0=z11x)
220     s_fixture_model_r2 = rf.Network(f=f, s=fixture_model_2r, z0=z11x)
221
222     # renormalize the S-parameter errorboxes to the original reference
223     # → impedance (assumed to be 50)
224     s_side1 = s_fixture_model_r1.copy()
225     s_side1.renormalize(50)
226     s_side2 = s_fixture_model_r2.copy()
227     s_side2.renormalize(50)
228 else:
229     # Use impedance method instead of time domain method
230     # Convert S-parameters to Z-parameters
231     z = rf.s2z(s_2xthru.s, s_2xthru.z0)
232     ZL = np.zeros(z.shape, dtype=complex)
233     ZR = np.zeros(z.shape, dtype=complex)
234
235     for i in range(len(z)):
236         ZL[i, 0, 0] = z[i, 0, 0] + z[i, 1, 0]
237         ZL[i, 0, 1] = 2 * z[i, 1, 0]
238         ZL[i, 1, 0] = 2 * z[i, 1, 0]
239         ZL[i, 1, 1] = 2 * z[i, 1, 0]
240
241         ZR[i, 0, 0] = 2 * z[i, 0, 1]
242         ZR[i, 0, 1] = 2 * z[i, 0, 1]
243         ZR[i, 1, 0] = 2 * z[i, 0, 1]
244         ZR[i, 1, 1] = z[i, 0, 1] + z[i, 1, 1]
245
246     # Convert Z-parameters back to S-parameters
247     SL = rf.z2s(ZL, s_2xthru.z0)
248     SR = rf.z2s(ZR, s_2xthru.z0)
249
250     s_side1 = rf.Network(f=f, s=SL, z0=50)
251     s_side2 = rf.Network(f=f, s=SR, z0=50)
252
253     return s_side1, s_side2
254
255 # ----- supporting functions -----
256
257 def make_symmetric(nonsymmetric):
258     """
259     Takes the nonsymmetric frequency domain input and makes it symmetric.
260     The function assumes the DC point is in the nonsymmetric data.
261
262     Parameters
263     -----

```

```

264     nonsymmetric : ndarray
265         Nonsymmetric frequency domain data
266
267     Returns
268     -----
269     symmetric : ndarray
270         Symmetric frequency domain data
271     """
272     symmetric_abs = np.vstack(
273         [np.abs(nonsymmetric), np.flip(np.abs(nonsymmetric[1:]), axis=0)]
274     )
275     symmetric_ang = np.vstack(
276         [np.angle(nonsymmetric), -np.flip(np.angle(nonsymmetric[1:]), axis
277             ↪ =0)]
278     )
279     symmetric = symmetric_abs * np.exp(1j * symmetric_ang)
280     return symmetric
281
282 def make_step(impulse):
283     """
284     Creates a step response from an impulse response.
285
286     Parameters
287     -----
288     impulse : ndarray
289         Impulse response
290
291     Returns
292     -----
293     step : ndarray
294         Step response
295     """
296     ustep = np.ones(len(impulse))
297     step = np.convolve(ustep, impulse)
298     step = step[: len(impulse)]
299     return step
300
301
302 def dc(s, f):
303     """
304     Calculates the DC point for S-parameters.
305
306     Parameters
307     -----
308     s : ndarray
309         S-parameter data
310     f : ndarray
311         Frequency data
312
313     Returns
314     -----
315     DCpoint : float
316         DC point value
317     """
318     DCpoint = 0.002 # seed for the algorithm
319     err = 1 # error seed
320     allowedError = 1e-12 # allowable error

```

```

321     cnt = 0
322     df = f[1] - f[0]
323     n = len(f)
324     t = np.linspace(-1 / df, 1 / df, n * 2 + 1)
325     ts = np.argmin(np.abs(t - (-3e-9)))
326     Hr = com_receiver_noise_filter(f, f[-1] / 2)
327
328     while err > allowedError:
329         h1 = make_step(
330             np.fft.fftshift(np.fft.ifft(make_symmetric(np.vstack([DCpoint,
331                 ↪ s * Hr]))))
332         )
333         h2 = make_step(
334             np.fft.fftshift(
335                 np.fft.ifft(make_symmetric(np.vstack([DCpoint + 0.001, s *
336                 ↪ Hr]))))
337             )
338         )
339         m = (h2[ts] - h1[ts]) / 0.001
340         b = h1[ts] - m * DCpoint
341         DCpoint = (0 - b) / m
342         err = np.abs(h1[ts] - 0)
343         cnt += 1
344
345     return DCpoint
346
347 def com_receiver_noise_filter(f, fr):
348     """
349     Receiver filter in COM defined by eq 93A-20.
350
351     Parameters
352     -----
353     f : ndarray
354         Frequency data
355     fr : float
356         Reference frequency
357
358     Returns
359     -----
360     Hr : ndarray
361         Filter response
362     """
363     fdfr = f / fr
364     Hr = 1.0 / (1 - 3.414214 * (fdfr) ** 2 + fdfr**4 + 1j * 2.613126 * (
365         ↪ fdfr - fdfr**3))
366     return Hr
367
368 def dc_interp(sin, f):
369     """
370     Enforces symmetry upon the first 10 points and interpolates the DC
371     ↪ point.
372
373     Parameters
374     -----
375     sin : ndarray
376         Input data

```

```

375     f : ndarray
376         Frequency data
377
378     Returns
379     -----
380     dc : float
381         DC point value
382     """
383     sp = sin[:10]
384     fp = f[:10]
385
386     snp = np.concatenate([np.conj(np.flip(sp)), sp])
387     fnp = np.concatenate([-np.flip(fp), fp])
388     fnew = np.concatenate([-np.flip(fp), [0], fp])
389     snew = interp.interp1d(fnp, snp, kind="cubic")(fnew)
390     dc = np.real(snnew[len(sp)])
391
392     return dc
393
394
395 def deembed_s_params(s_fixture_dut_fixture, s_side1, s_side2):
396     """
397     De-embeds the S-parameters of a DUT from measurements that include test
398     ↪ fixtures.
399
400     Parameters
401     -----
402     s_fixture_dut_fixture : rf.Network
403         S-parameter network object of the DUT with fixtures
404     s_side1 : rf.Network
405         S-parameter network object of the error box for port 1
406     s_side2 : rf.Network
407         S-parameter network object of the error box for port 2
408
409     Returns
410     -----
411     s_deembedded_dut : rf.Network
412         De-embedded S-parameter network object of the DUT
413     """
414     # Create T-parameters for the error boxes
415     t_side1 = s_side1.s2t
416     t_side2 = s_side2.s2t
417
418     # Create T-parameters for the fixture+DUT+fixture
419     t_fixture_dut_fixture = s_fixture_dut_fixture.s2t
420
421     # De-embed the DUT
422     t_dut = np.zeros(t_fixture_dut_fixture.shape, dtype=complex)
423
424     # T_DUT = inv(T_side1) * T_fixture_dut_fixture * inv(T_side2)
425     for i in range(len(t_fixture_dut_fixture)):
426         t_dut[i] = (
427             np.linalg.inv(t_side1[i])
428             @ t_fixture_dut_fixture[i]
429             @ np.linalg.inv(t_side2[i])
430         )
431
432     # Convert back to S-parameters

```

```
432 s_deembedded_dut = s_fixture_dut_fixture.copy()
433 s_deembedded_dut.s = rf.t2s(t_dut)
434
435 return s_deembedded_dut
```

Code Listing G.5: Lab 8: High-Pass Filter "Open-Short-Thru" S-Parameter De-Embedding Method (IEEE std. P370)

```

1 import skrf as rf
2 import numpy as np
3 import scipy.linalg
4 import matplotlib.pyplot as plt
5
6 open_standard = rf.Network('Open.s2p')
7 short_standard = rf.Network('Short.s2p')
8 thru_standard = rf.Network('Thru.s2p')
9 dut = rf.Network('hpf.s2p')
10
11 def deembed_osp(dut, open_std, short_std, thru_std):
12     thru_half = thru_std.copy()
13     thru_half.s = np.zeros_like(thru_std.s)
14     for i in range(len(thru_std.f)):
15         s = thru_std.s[i]
16         s_3d = s.reshape(1, *s.shape)
17         t = rf.s2t(s_3d)
18         t_half = scipy.linalg.sqrtm(t[0])
19         t_half_3d = t_half.reshape(1, *t_half.shape)
20         s_half = rf.t2s(t_half_3d)[0]
21         thru_half.s[i] = s_half
22
23     y_open = open_std.y
24     z_short = short_std.z
25     y_parasitic = y_open
26     y_short = short_std.y
27     y_short_corrected = y_short - y_parasitic
28     z_parasitic = rf.network.y2z(y_short_corrected)
29
30     dut_y = dut.y
31     dut_y_corrected = dut_y - y_parasitic
32     dut_z = rf.network.y2z(dut_y_corrected)
33     dut_z_corrected = dut_z - z_parasitic
34
35     dut_corrected = rf.Network(s=rf.z2s(dut_z_corrected),
36                                frequency=dut.frequency)
37     return dut_corrected
38
39 hpf_deembedded = deembed_osp(dut, open_standard, short_standard,
40                               ➔ thru_standard)
41 hpf_deembedded.write_touchstone('hpf_deembedded.s2p')
42
43 plt.figure(figsize=(12, 8))
44
45 plt.subplot(2, 1, 1)
46 plt.title('HPF - OST - S21 - Transmission')
47 dut.plot_s_db(m=0, n=1, label='Original')
48 hpf_deembedded.plot_s_db(m=0, n=1, label='OST De-embedded')
49 plt.grid(True)
50 plt.legend()
51
52 plt.subplot(2, 1, 2)
53 plt.title('HPF - OST De-Embed - S11 - Reflection')
54 dut.plot_s_db(m=0, n=0, label='Original')
55 hpf_deembedded.plot_s_db(m=0, n=0, label='OST De-embedded')

```



```
55 plt.grid(True)
56 plt.legend()
57
58 plt.tight_layout()
59 plt.savefig('hpf_deembedded_comparison.png')
60 plt.show()
```

Code Listing G.6: Lab 8: High-Pass Filter "Thru" S-Parameter De-Embedding Method (IEEE std. P370)

```

1 import skrf as rf
2 import ieee_p370_2x_thru_alt
3 # from ieee_p370_2x_thru_alt import deemed_s_params
4 import numpy as np
5
6 def deemed_s_params(s_fixture_dut_fixture, s_side1, s_side2):
7     """
8     De-embeds the S-parameters of a DUT from measurements that include test
9     ↪ fixtures.
10
11     Parameters
12     -----
13     s_fixture_dut_fixture : rf.Network
14         S-parameter network object of the DUT with fixtures
15     s_side1 : rf.Network
16         S-parameter network object of the error box for port 1
17     s_side2 : rf.Network
18         S-parameter network object of the error box for port 2
19
20     Returns
21     -----
22     s_deembedded_dut : rf.Network
23         De-embedded S-parameter network object of the DUT
24     """
25     # Create T-parameters for the error boxes
26     t_side1 = rf.s2t(s_side1.s)
27     t_side2 = rf.s2t(s_side2.s)
28
29     # Create T-parameters for the fixture+DUT+fixture
30     t_fixture_dut_fixture = rf.s2t(s_fixture_dut_fixture.s)
31
32     # De-embed the DUT
33     t_dut = np.zeros(t_fixture_dut_fixture.shape, dtype=complex)
34
35     #  $T_{DUT} = \text{inv}(T_{side1}) * T_{fixture\_dut\_fixture} * \text{inv}(T_{side2})$ 
36     for i in range(len(t_fixture_dut_fixture)):
37         t_dut[i] = (
38             np.linalg.inv(t_side1[i])
39             @ t_fixture_dut_fixture[i]
40             @ np.linalg.inv(t_side2[i])
41         )
42
43     # Convert back to S-parameters
44     s_deembedded_dut = s_fixture_dut_fixture.copy()
45     s_deembedded_dut.s = rf.t2s(t_dut)
46
47     return s_deembedded_dut
48
49 # 1. Load your 2x-thru calibration measurement
50 s_2xthru = rf.Network('Thru.s2p')
51
52 # 2. Generate the error boxes (fixture models) from the 2x-thru
53 # Modified to use use_ifft=False to avoid the problematic IFFT calculation
54 s_side1, s_side2 = ieee_p370_2x_thru_alt.ieee_p370_2x_thru_alt(s_2xthru,
55     ↪ use_ifft=False)

```

```

54
55 # 3. Load your DUT measurement (with fixtures)
56 s_fixture_dut_fixture = rf.Network('hpf.s2p')
57
58 # 4. De-embed the fixture effects to get the actual DUT response
59 s_deembedded_dut = deembed_s_params(s_fixture_dut_fixture, s_side1, s_side2
    ↪ )
60
61 # 5. Save the de-embedded DUT S-parameters to a file
62 s_deembedded_dut.write_touchstone('hpf_ieee_deembedded_dut.s2p')
63
64 # Optional: Plot the results to verify
65 import matplotlib.pyplot as plt
66
67 plt.figure(figsize=(10, 6))
68 plt.title('HPF S-parameters Before and After De-embedding')
69
70 # Plot S11 before and after de-embedding
71 plt.plot(s_fixture_dut_fixture.f/1e9, 20*np.log10(np.abs(
    ↪ s_fixture_dut_fixture.s[:,0,0])),
72         label='S11 with fixtures')
73 plt.plot(s_deembedded_dut.f/1e9, 20*np.log10(np.abs(s_deembedded_dut.s
    ↪[:,0,0])),
74         label='S11 de-embedded')
75
76 # Plot S21 before and after de-embedding
77 plt.plot(s_fixture_dut_fixture.f/1e9, 20*np.log10(np.abs(
    ↪ s_fixture_dut_fixture.s[:,1,0])),
78         label='S21 with fixtures')
79 plt.plot(s_deembedded_dut.f/1e9, 20*np.log10(np.abs(s_deembedded_dut.s
    ↪[:,1,0])),
80         label='S21 de-embedded')
81
82 plt.xlabel('Frequency (MHz)')
83 plt.ylabel('Magnitude (dB)')
84 plt.legend()
85 plt.grid(True)
86 plt.show()

```